

Input:  $V_p \cos \omega t$

Output:  $\frac{k V_p}{\sqrt{1 + \frac{\omega^2 k^2}{\omega_u^2}}} \cdot \cos \left[ \omega t - \tan^{-1} \left( \frac{\omega k}{\omega_u} \right) \right]$

①

For low freq:-

$\omega \ll \frac{\omega_u}{k}$

Output:  $k V_p$

So we neglected  $\frac{\omega^2 k^2}{\omega_u^2}$

$k V_p \cos \left( \omega t - \frac{\omega k}{\omega_u} \right)$

$= k V_p \cos \left[ \omega \left( t - \frac{k}{\omega_u} \right) \right]$

Amp  
(gain = k)

delay  $\Rightarrow \frac{k}{\omega_u}$

②

For high freq:-

$\omega \gg \frac{\omega_u}{k}$

Output =  $\frac{k V_p}{\sqrt{\frac{k^2 \omega^2}{\omega_u^2}}} \cos \left( \omega t - \tan^{-1} \left( \frac{\omega k}{\omega_u} \right) \right)$

neglecting '1' here

Very large

So,  $\tan^{-1} \left( \frac{\omega k}{\omega_u} \right) \approx \frac{\pi}{2}$

So, output =  $\frac{k V_p}{\sqrt{\frac{k^2 \omega^2}{\omega_u^2}}} \cdot \cos \left( \omega t - \frac{\pi}{2} \right)$

Output =  $V_p \frac{\omega_u}{\omega} \cos \left( \omega t - \frac{\pi}{2} \right)$

→ The output is independent of 'k'.

→ The gain is arbitrary & phase lag of  $\frac{\pi}{2}$ .

Summary:-

① At low frequencies ( $\omega < \frac{\omega_u}{k}$ )

Amp working properly

$$\text{Output} \approx kV_p \cos\left(\omega t - \frac{k}{\omega_u}\right)$$

Ideal gain  $\Rightarrow$  Independent of  $\omega_u$ , the parameter of the integrator

Delay ' $\frac{k}{\omega_u}$ '

Amp. not working properly.

② At High frequencies ( $\omega \gg \frac{\omega_u}{k}$ )

$$\text{Output} \approx \frac{\omega_u}{\omega} V_p \cos\left(\omega t - \frac{\pi}{2}\right)$$

Arbitrary gain:- independent of  $k$ , the gain of amp.

Delay ' $\frac{\pi}{2}$ '

Usable range of

that's why  $\frac{\omega_u}{k} \rightarrow \text{Bandwidth freq.}$

# Frequency domain analysis


Bandwidth of system

The amp. is usable for frequencies below  $(\frac{\omega_u}{k})$

For higher bandwidth, use an integrator with a higher  $\omega_u$ .

Time domain	Frequency domain
Step Response: $V_o(t) = k V_x [1 - \exp(-\frac{\omega_u t}{k})]$	Pole: $-\omega_u/k$ $\rightarrow$ Bandwidth = $\frac{\omega_u}{k}$
Time constant = $k/\omega_u$	

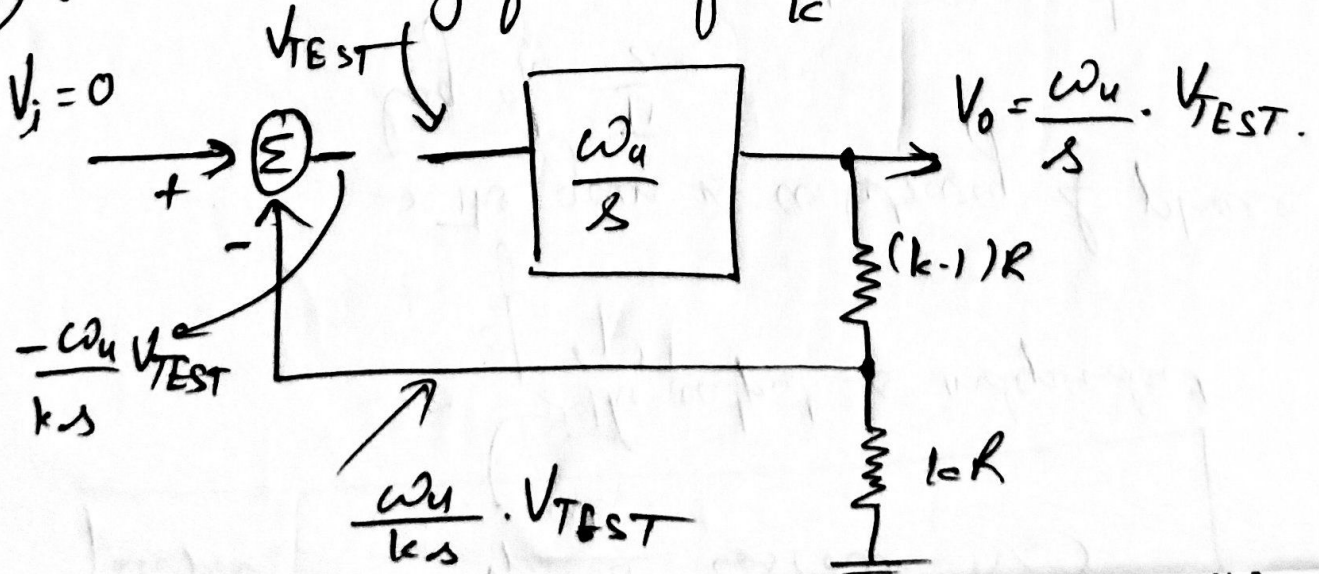① What is the significance of  $\frac{\omega_u}{k}$ ?



$$V_{Return} = -\frac{\omega_u}{k \cdot s} V_{TEST}$$


→ Loop gain is the quantity that quantifies the amount of feedback.

$$\text{Loop Gain} = \frac{V_{\text{Return}}}{V_{\text{TEST}}} = -\frac{\omega_u}{k_s} = -L(s)$$

$L(s) \rightarrow \text{Loop gain}$

Now, for our case

$$L(s) = \frac{\omega_u}{k_s}$$

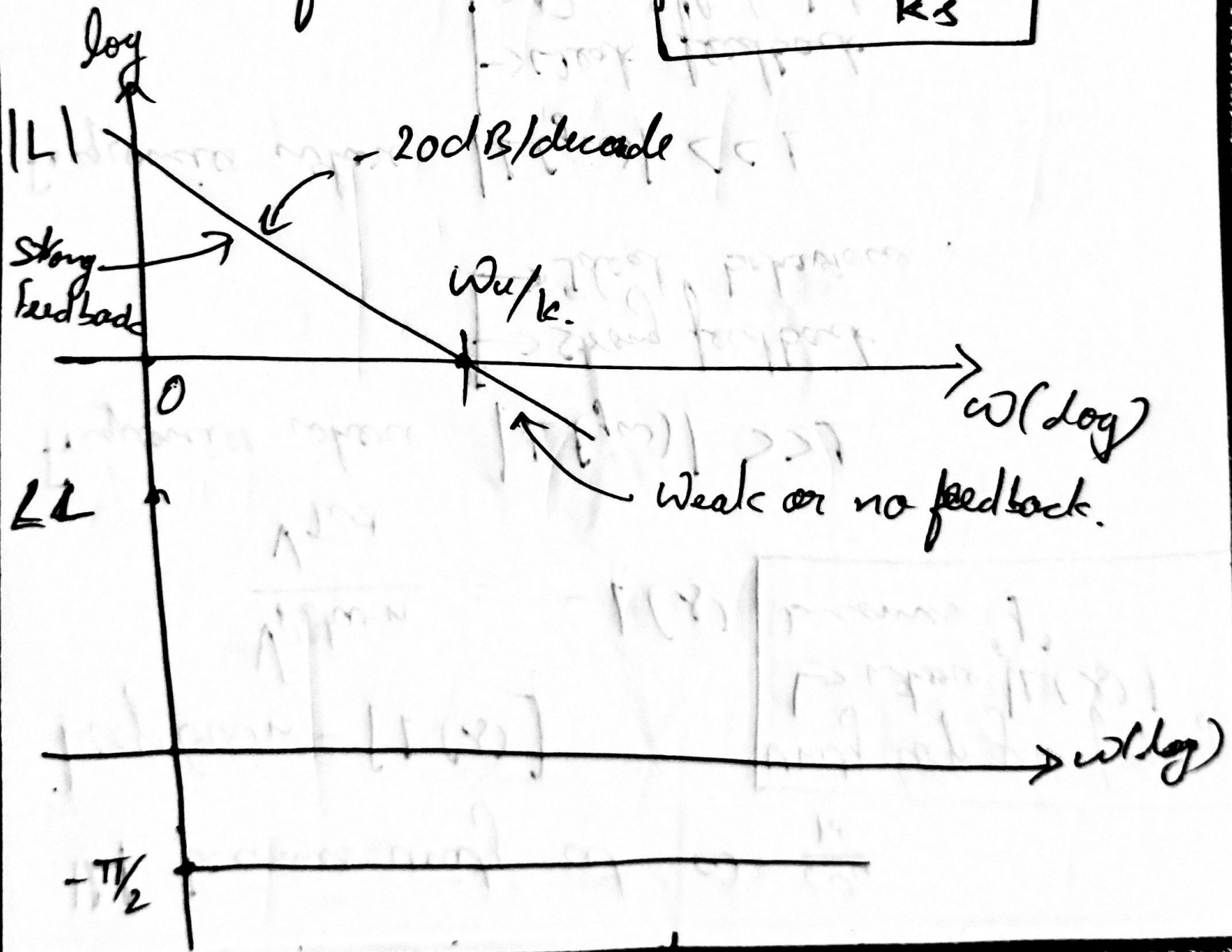



$|H|$  becomes unity at  $\omega = \frac{\omega_u}{1c}$

Loop Gain:-  $[L(s)]$

$$\frac{V_{\text{Return}}}{V_{\text{Test}}} = -L(s)$$

Unity loop gain frequency  
→ where  $|L(s)|$  becomes '1'

Frequencies where  $|L(j\omega)| \gg 1$

→ Strong feedback  
→ Ideal behaviour.


Frequencies where  $|L(j\omega)| \ll 1$

→ Weak feedback  
→ Non-Ideal behaviour.

→ Now combining the  $\Sigma$  &  $\boxed{\frac{\omega_u}{s}}$  and making one block.


→ Difference between input & feedback & }

→ Integrates the difference

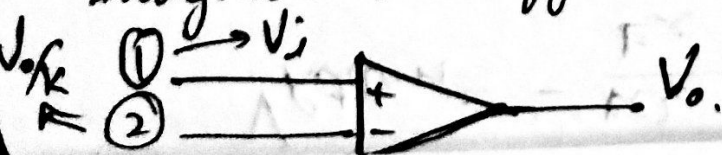

known as Op-amp.

Now,

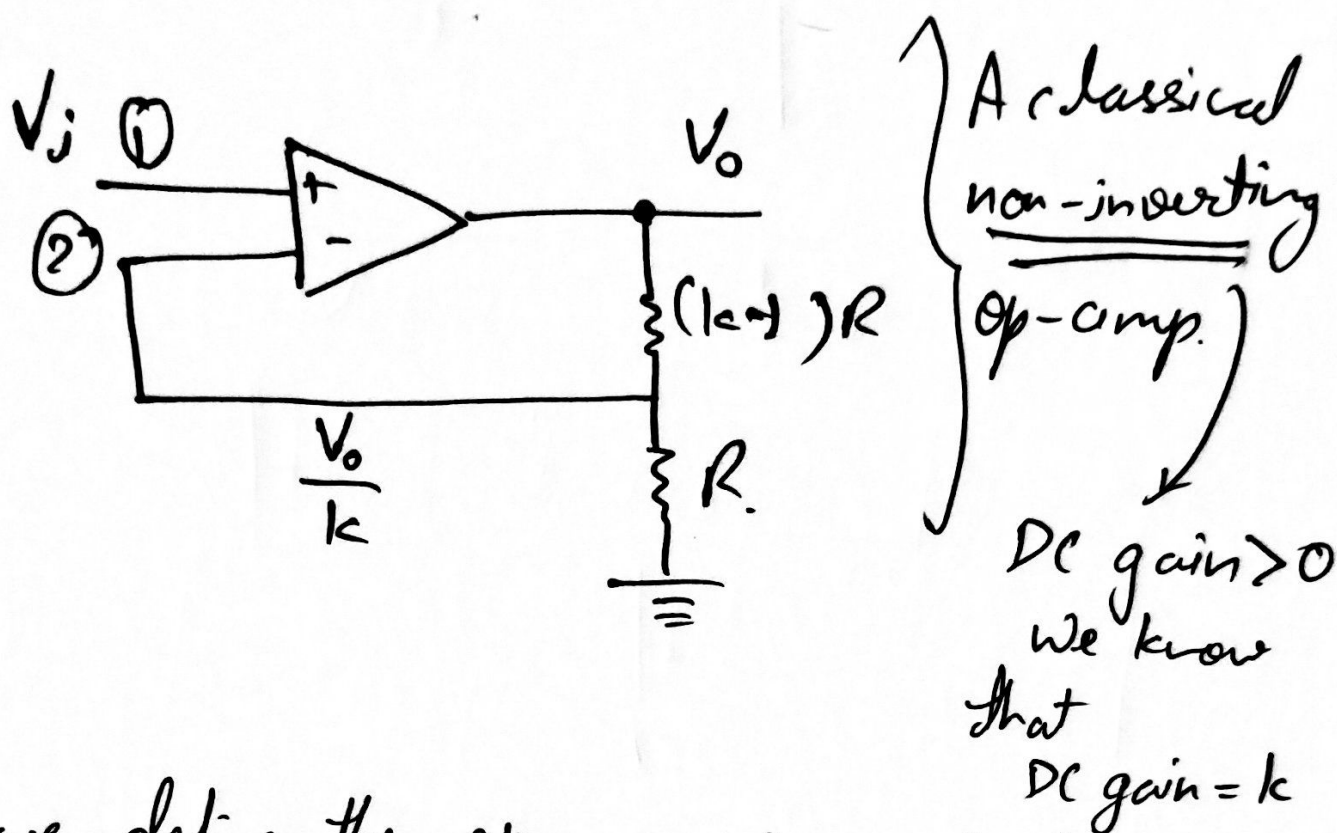

→ And we define the op-amp using a single parameter ' $\omega_u$ '

→ Unity gain frequency of the op-amp.

$$\boxed{\frac{V_o(s)}{V_i(s)} = \frac{k}{1 + \frac{s k}{\omega_u}}}$$

→ BW

Ideal op-amp:- Bandwidth =  $\frac{\omega_u}{k}$

Now, if  $\omega_u = \infty \rightarrow BW = \infty$

So, →  $\boxed{\frac{V_o(s)}{V_i(s)} = k}$