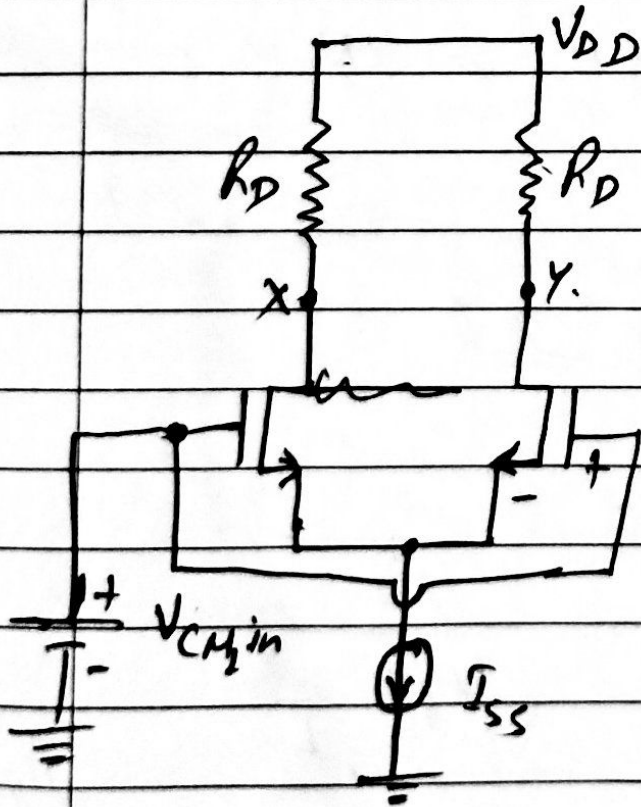


Additional Analysis of MOS Differential Pair:-

* Summary of the Results



Now,

$$V_X = V_{DD} - R_D I_{D1}$$

$$V_Y = V_{DD} - R_D I_{D2}$$

$$V_X - V_Y = -R_D [I_{D1} - I_{D2}]$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{th})^2$$

$$V_{GS} = \sqrt{\frac{2 I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{th}$$

$$V_{GS1} = V_{GS2} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} + V_{th}$$


Now,

$$V_{ov} = V_{GS1} - V_{th} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

- Equilibrium Overdrive

Teacher's Signature: _____


②

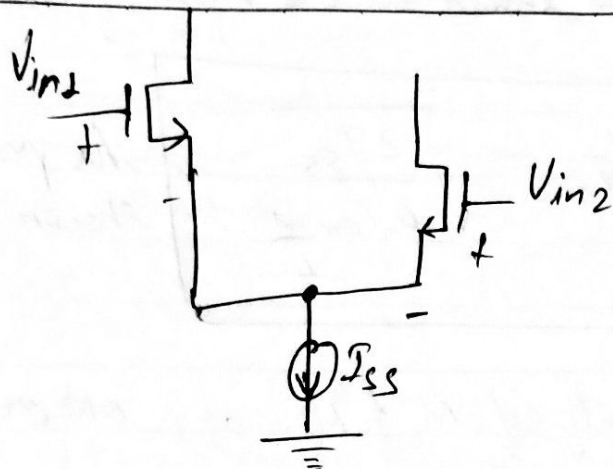

Min. $|V_{in1} - V_{in2}|$ necessary to turn off one side:

$$\sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

③

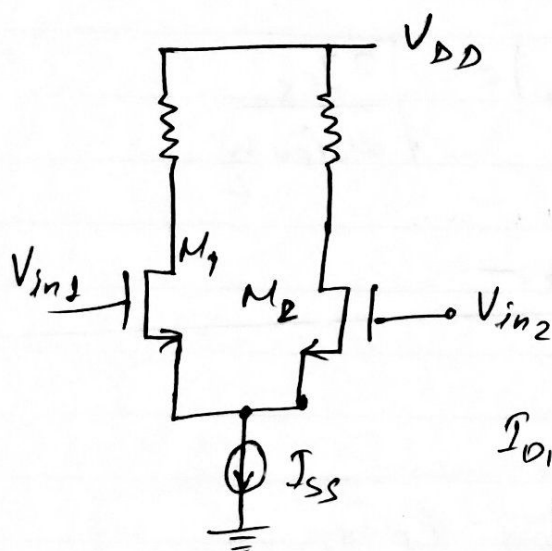


$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{in1} - V_{in2}) \sqrt{\frac{4 I_{SS} - (V_{in1} - V_{in2})^2}{\mu_n C_{ox} \frac{W}{L}}}$$

Valid if M_1 & M_2 are ON or near turning OFF.

→ If $V_{GS} < V_{th}$ of any transistor then it won't be valid.

If $V_{in1} - V_{in2} = 0 \rightarrow I_{D1} = I_{D2}$

→ Validity of the eqⁿ only if:-

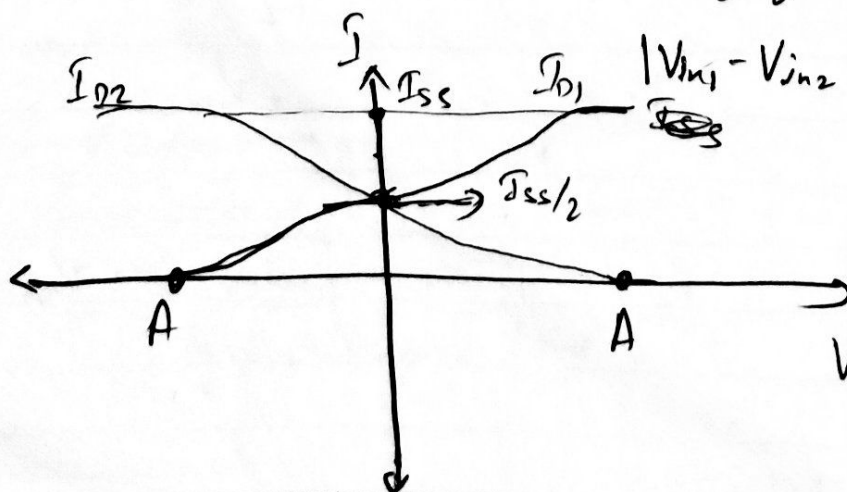


$$|V_{in1} - V_{in2}| \leq \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

If $V_{in1} - V_{in2} = \pm \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$ then $I_D = 0$ at point A.

⑤.
$$V_x - V_y = -\frac{R_D}{2} \ln \cos\left(\frac{\omega}{L}\right) (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\ln \cos \frac{\omega}{L}}} - (V_{in1} - V_{in2})^2$$

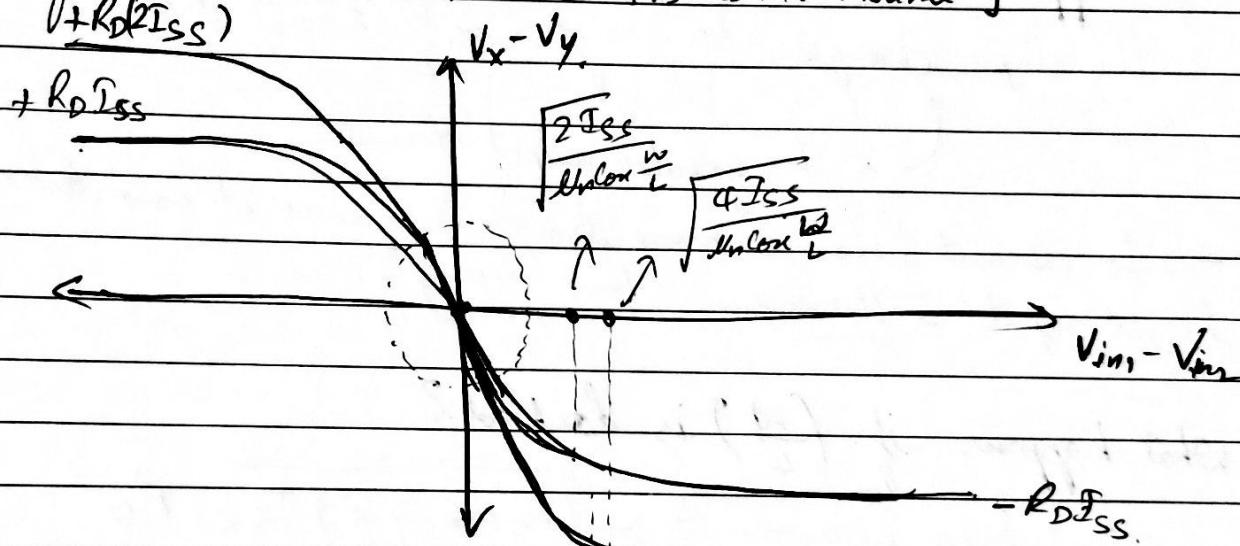Let's focus on when $(V_{in1} - V_{in2})$ is small [Assume]



Approximate $(V_{in1} - V_{in2})$ by straight line :- $= R_D(2I_{SS})$

If
$$(V_{in1} - V_{in2})^2 < \frac{4I_{SS}}{\ln \cos \frac{\omega}{L}}$$

So,
$$V_x - V_y = -\frac{R_D}{2} \ln \cos\left(\frac{\omega}{L}\right) (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\ln \cos \frac{\omega}{L}}}$$
very small

$$\approx -\frac{R_D}{2} \ln \cos\left(\frac{\omega}{L}\right) \sqrt{\frac{4I_{SS}}{\ln \cos \frac{\omega}{L}}} [V_{in1} - V_{in2}]$$

$$\approx -R_D \sqrt{\frac{I_{SS} \ln \cos \frac{\omega}{L}}{L}} = -\sqrt{\frac{\ln \cos \frac{\omega}{L} I_{SS}}{L}} \times R_D [V_{in1} - V_{in2}]$$

So,

$$\text{slope} = - \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS} R_D}$$

→ will give gain of the circuit.

Examples

① What happens when ~~tail~~ tail current (I_{SS}) is doubled?

→ The slope changes to $-\sqrt{\mu_n C_{ox} \frac{W}{L} (2I_{SS}) R_D}$

→ The greater output change.

→ The circuit becomes more linear because it can take more larger input difference without 'dying'.

Quiz
② What happens if $\left(\frac{W}{L}\right)$ is doubled?

→ The slope changes to $-\sqrt{\mu_n C_{ox} 2\left(\frac{W}{L}\right) I_{SS} R_D}$

→ But $R_D I_{SS}$ will remain same.

→ The circuit becomes less linear because it can take only a smaller input difference before it 'dies'.