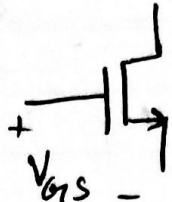



# \* Current Mirrors

## Basic Concept

→ Problem of biasing current sources

① Issue ①


$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{th})^2$$

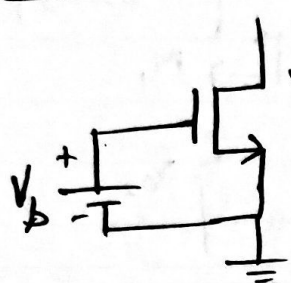
$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_b - V_{th})^2$$


→ Vary with temp.

② Issue ②

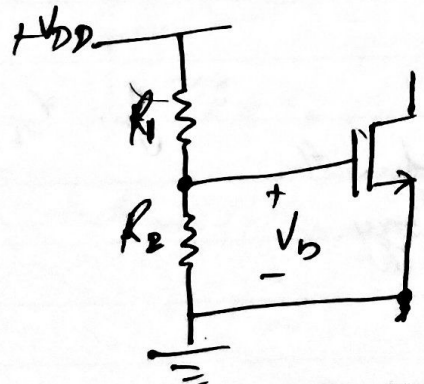How generate  $V_b$  from  $V_{DD}$ : → main supply voltage.




$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) \left[ \frac{R_2 V_{DD}}{R_1 + R_2} - V_{th} \right]^2$$

Supply dependent.

Now the solution [Current Mirror]:-

→ First we build one 'golden' circuit current source using a 'Bandgap' circuit.

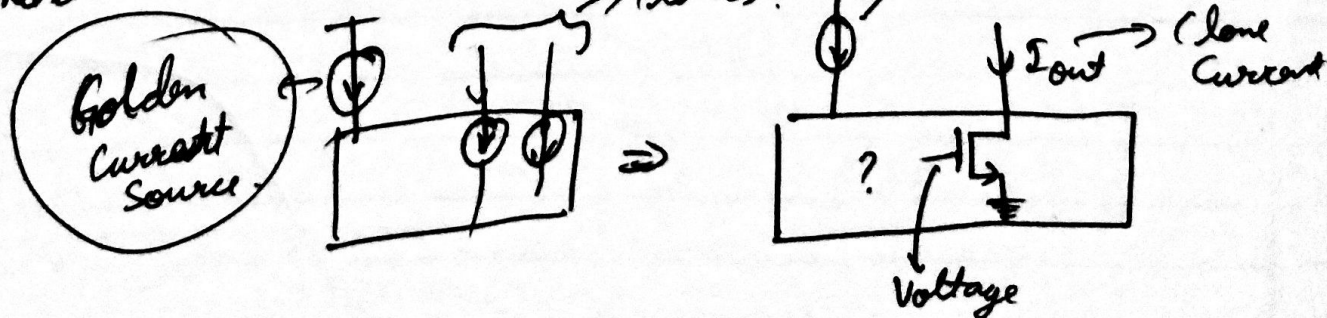→ Next we clone this current source to build many others.




# Quiz

EXPT. NO. NAME

M T W T F S S  
Page No. YOUVA  
Date

$$V = I_{ref} R_1$$

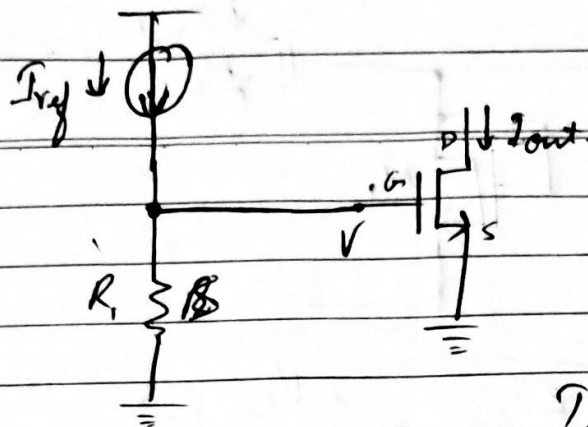


$$I_{out} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) [V_G - V_{th}]^2$$

$$I_{out} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) [I_{ref} R_1 - V_{th}]^2$$

→ Vary with temp

## Observations:-


①

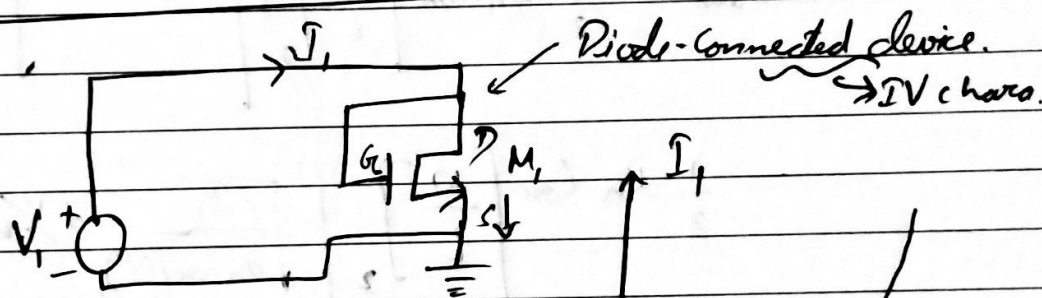

→ If  $M_1$  is on it is in saturation.

$$V_G > V_{th}$$


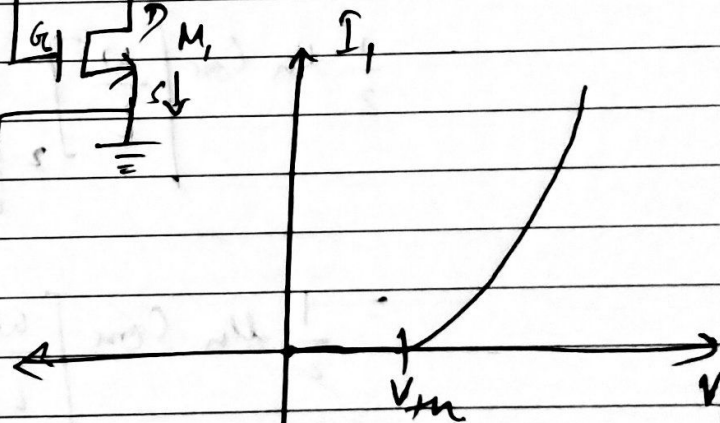
$$V_1 \leftarrow V_{DS} > (V_{GS} - V_{th})$$



$$\text{At Sat :- } I_1 = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) [V_1 - V_{th}]^2$$


$$(V_1 \gg V_{th})$$
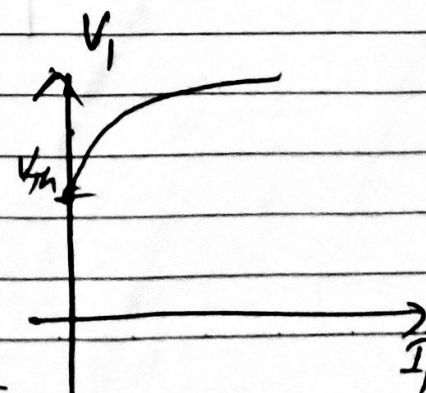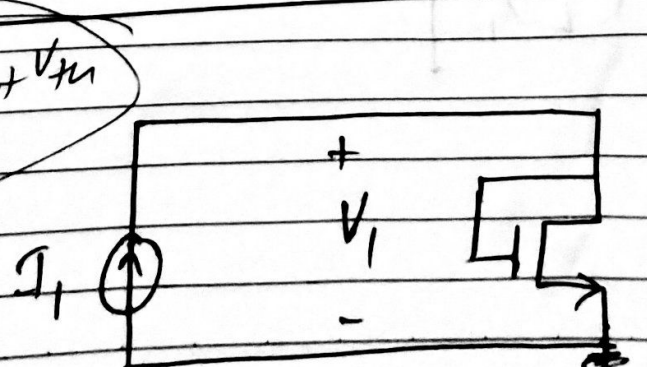
$$V_1 = \frac{2 I_1}{\mu_n C_{ox} \left( \frac{W}{L} \right)}$$



Signature:

②

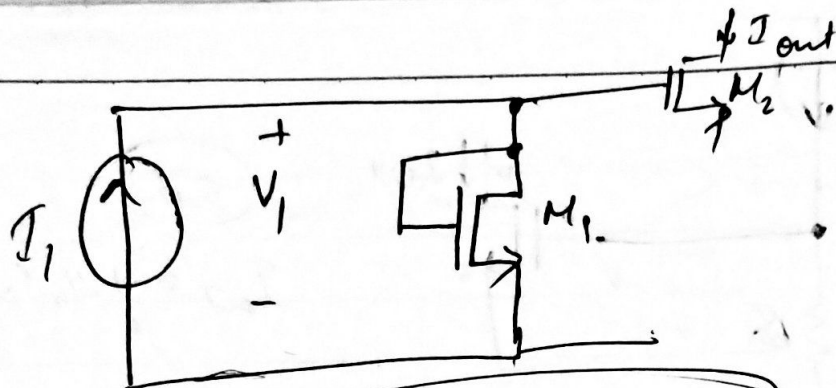

$$V_1 = \sqrt{\frac{2I_1}{\mu_n \text{ Cox } \left(\frac{W}{L}\right)_1}} + V_{th}$$

$$\text{So, } I_{out} = \frac{1}{2} \mu_n \text{ Cox } \left[\frac{W}{L}\right]_2 \left[V_1 - V_{th}\right]^2$$

$$= \frac{1}{2} \mu_n \text{ Cox } \left[\frac{W}{L}\right]_2 \left[\sqrt{\frac{2I_1}{\mu_n \text{ Cox } \left(\frac{W}{L}\right)_1}} + V_{th} - V_{th}\right]^2$$

$$= \frac{1}{2} \mu_n \text{ Cox } \left[\frac{W}{L}\right]_2 \left[\frac{2I_1}{\mu_n \text{ Cox } \left(\frac{W}{L}\right)_1}\right]$$

$$= \left[\frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1}\right] \times I_1$$



# Current Mirror

EXPT.  
NO.


NAME

M T W T F S S

Page No.

Date

YOUVA

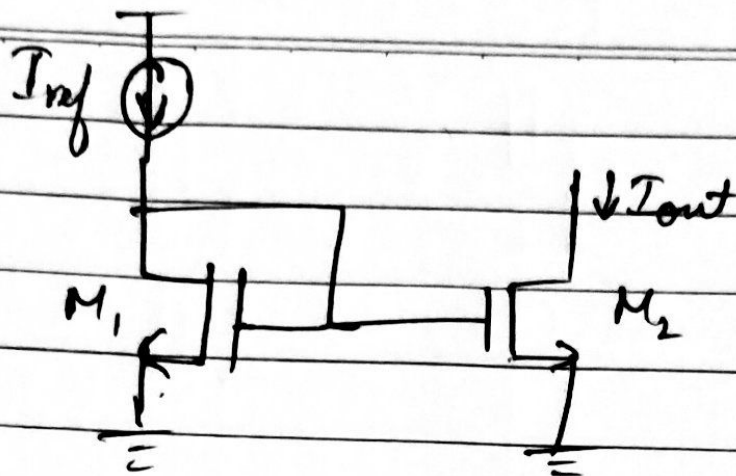

→  $I_{out}$  &  $I_{ref}$  is only related by  $\left(\frac{W}{L}\right)$  ratios of both transistors

$$\text{i.e., } I_{out} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} \times I_{ref.}$$

$L_1 = L_2$  always

& Select  $W_1$  &  $W_2$  accordingly.