


Negative feedback comp

RC filter.

$$V_i \rightarrow DC$$

$$V_o = k V_i \text{ in steady state.}$$
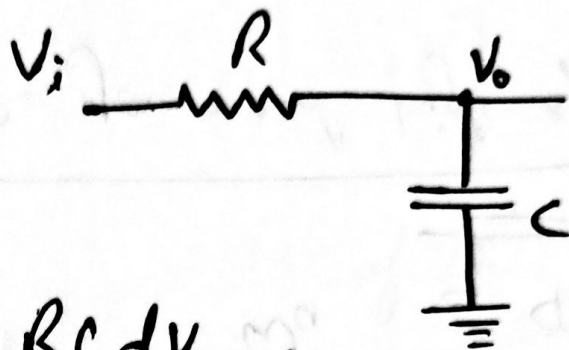
$$\frac{1}{\omega_u} \frac{dV_o}{dt} = V_i - \frac{V_o}{k}$$



$$RC \frac{dV_o}{dt} = V_i - V_o$$


1st order DE.

Solution:-


$$V_o(t) = V_o(0) \cdot \exp\left(-\frac{\omega_u}{k} \cdot t\right) + k V_i \left[1 - \exp\left(-\frac{\omega_u}{k} \cdot t\right)\right]$$

- Same behaviour as 1st order RC filter.
- Till now we worked with a constant input.
- Now we'll work on step input & sinusoidal input [variable input].

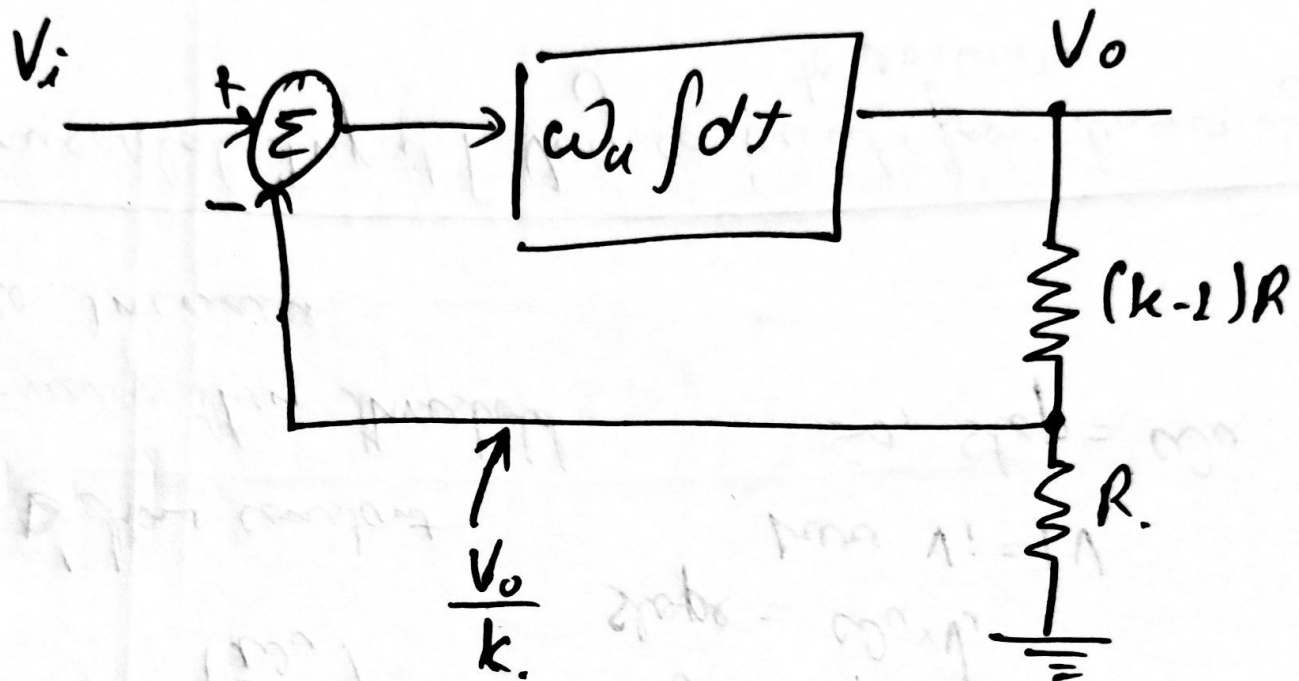* Response of negative feedback comp. to a step input.



Waveforms

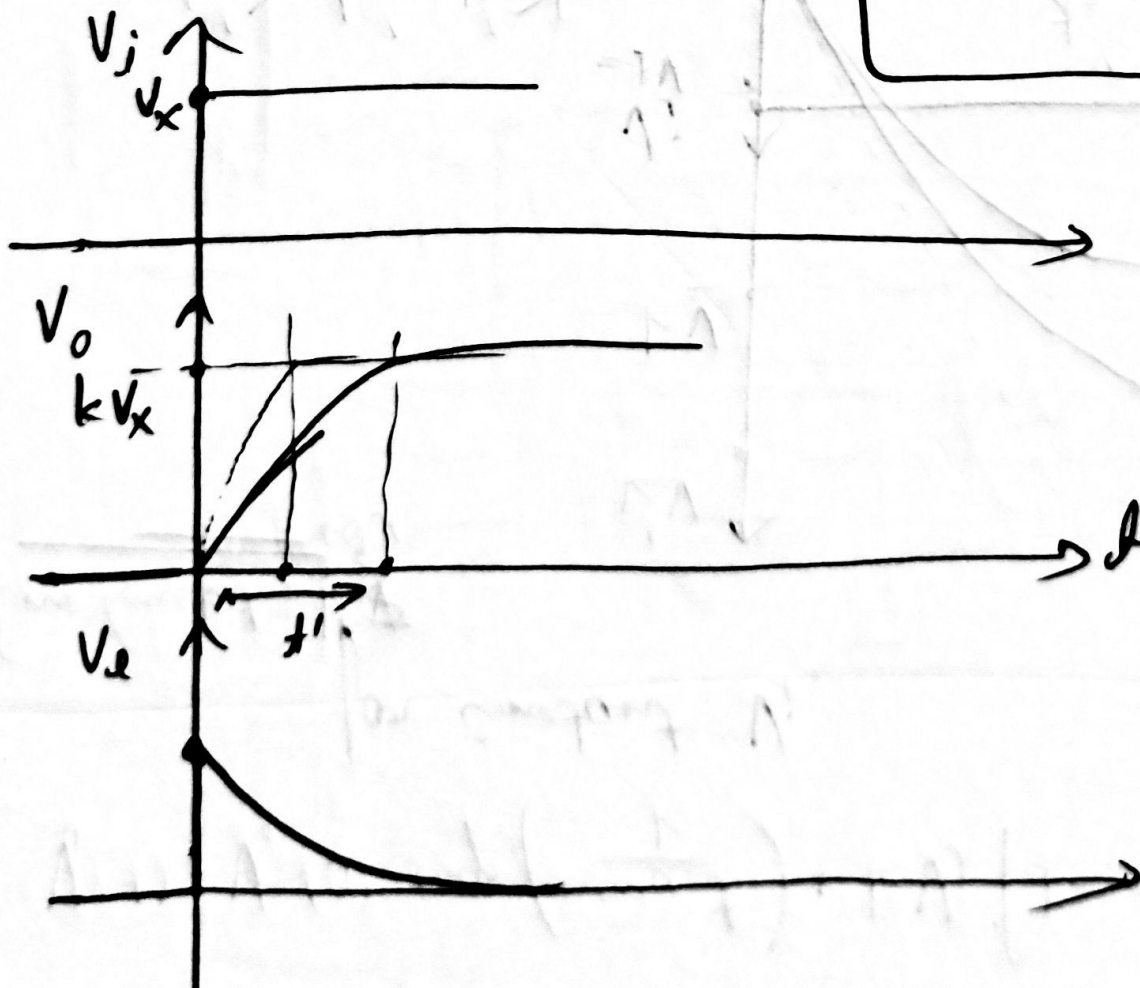

Threshold $\leftarrow t' = 4.6 \left(\frac{1}{\omega_u} \right)$
to reach 99% of steady state


→ Higher value of ω_u , you will be having faster approach to steady state

→ Smaller energy (area) of the error $V_i - V_o/k$

$$V(t) = V_o(0) \exp\left(-\frac{\omega_u t}{k}\right) + k V_i \left[1 - \exp\left(-\frac{\omega_u t}{k}\right)\right]$$

for constant V_i .

Time Constant = $\frac{k}{\omega_u}$

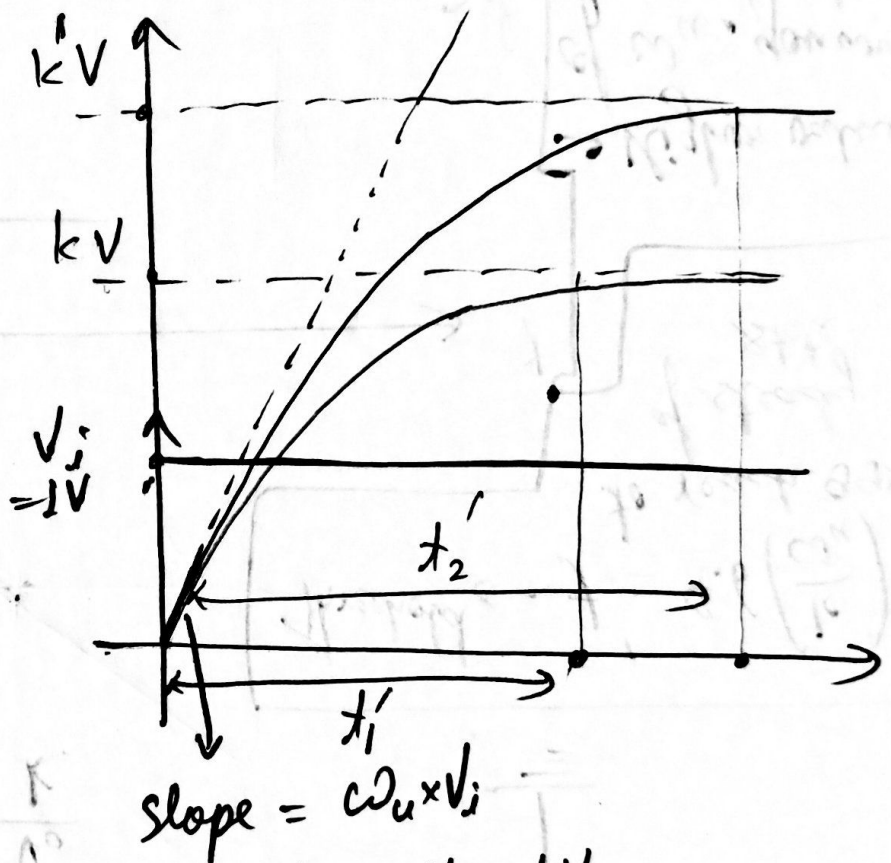

Since $t'_2 > t'_1 \rightarrow k' > k$.


$$t' = 4.6 \left(\frac{k}{\omega_u}\right)$$

→ If time constant increases then threshold also increases.

here $V_i = 1V$


So, $\text{slope} = \omega_u$.

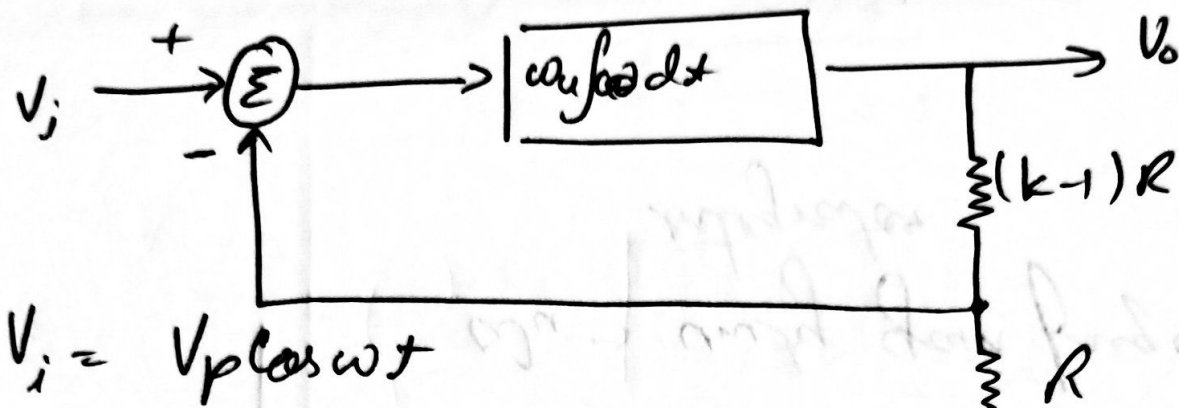* Sinusoidal Input [Very convenient for linear system to evaluate]




Time domain

Freq. domain

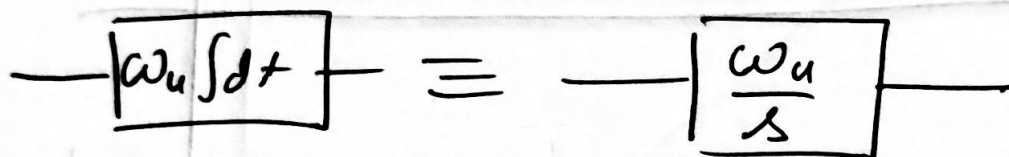

Integrator

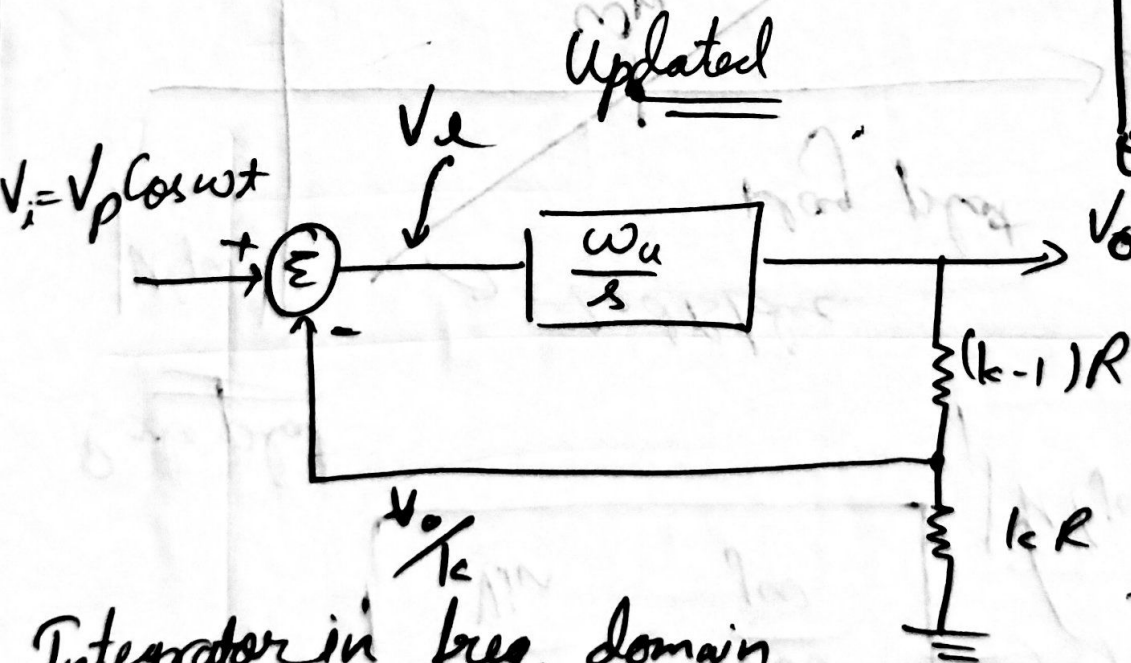


$$V_o = \left(V_i - \frac{V_o}{k} \right) \frac{\omega_u}{s}$$

$$\frac{V_i \omega_u}{s} = V_o \left[\frac{\omega_u}{ks} + 1 \right]$$

$$\frac{V_o}{V_i} = \frac{\omega_u/s}{\frac{\omega_u}{ks} + 1}$$

Cont. next page

Integrator in freq. domain

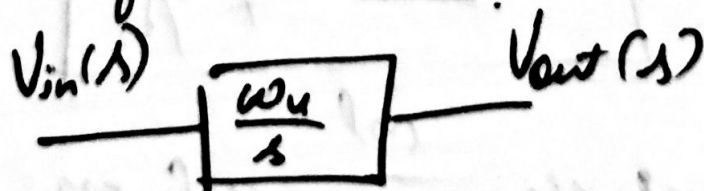

$$V_{out}(s) = \frac{\omega_u}{s} \cdot V_{in}(s)$$

$$V_{out}(t) = \omega_u \int V_{in}(t) dt$$

Substitute $s = j\omega$


$$V_{out}(j\omega) = \frac{\omega u}{j\omega} \cdot V_{in}(j\omega)$$

$$\frac{V_{out}}{V_{in}} = \frac{\omega u}{j\omega}$$

Transfer function

$$H(j\omega) = \frac{\omega u}{j\omega}$$

Bode plot

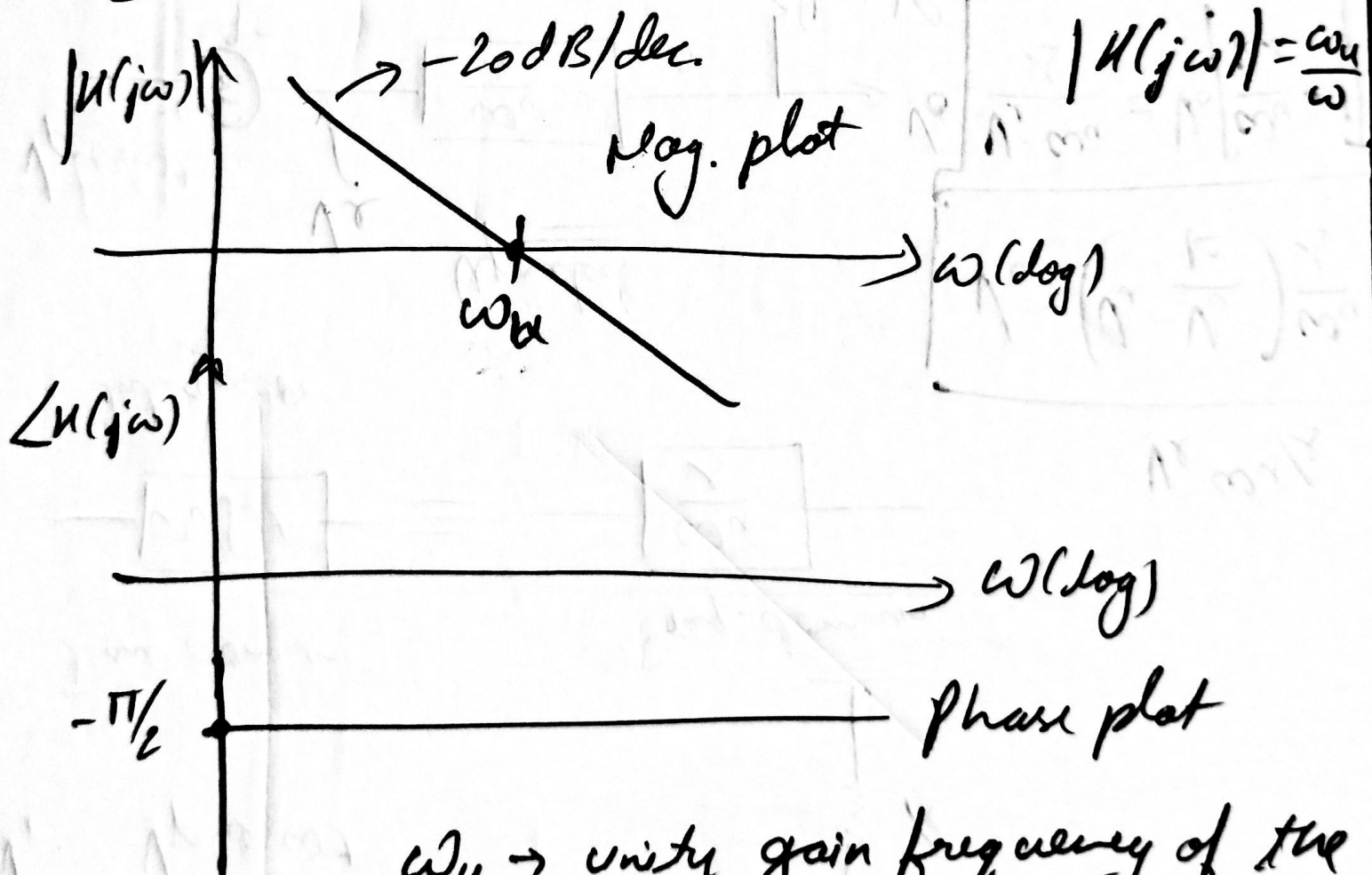

$\omega_u \rightarrow$ unity gain frequency of the integrator.

$$H(s) = \frac{V_o}{V_i} = \frac{\omega_u/s}{\left(\frac{\omega_u}{k s} + 1\right)}$$

x by $\frac{k s}{\omega_u}$

Transfer function.

$$H(s) = \frac{V_o}{V_i} = \frac{k}{\left(1 + \frac{k s}{\omega_u}\right)}$$

Now, $H(0) = k$ → Input is constant

DC gain of amp. is 'k' [Already known]

$$\frac{V_o}{V_i} = \frac{k}{1 + \frac{k s}{\omega_u}}$$


Pole at $-\frac{\omega_u}{k}$

$$1 + \frac{k s}{\omega_u} = 0$$

$$s = -\frac{\omega_u}{k}$$

1st order system with single pole.

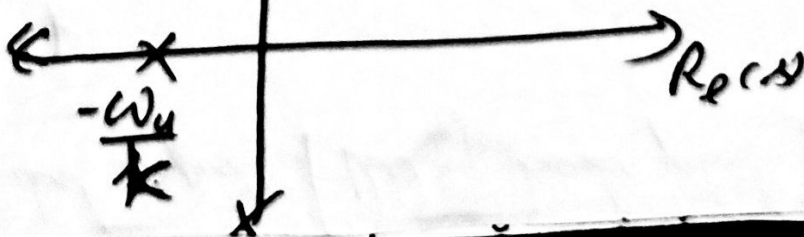→ For the system to be stable the pole should be in left side.



Analysis of Sinusoidal input [Using bode plot]


$$U(s) = \frac{k}{1 + s \frac{k}{\omega_u}}$$

$$U(j\omega) = \frac{k}{1 + j\omega \frac{k}{\omega_u}}$$

$$|U(j\omega)| = \frac{k}{\sqrt{1 + \frac{k^2 \omega^2}{\omega_u^2}}}$$

Revise
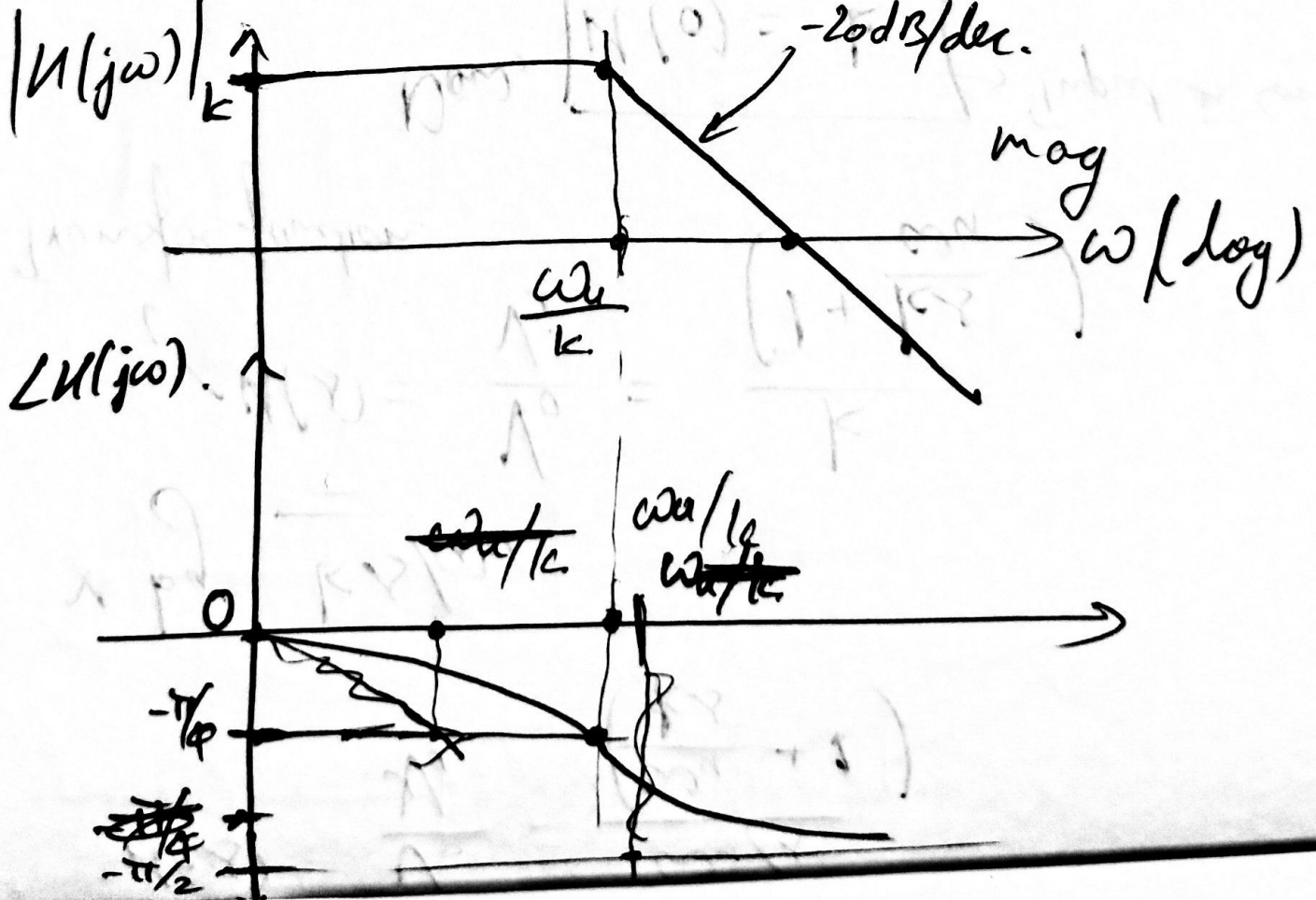
$$\angle U(j\omega) = -\tan^{-1}\left(\frac{\omega k}{\omega_u}\right)$$



Approximation

$$|U(j\omega)| \begin{cases} k, & \omega = 0 \\ \frac{k}{\sqrt{\frac{k^2 \omega^2}{\omega_u^2} + 1}}, & \omega \rightarrow \text{very large} \end{cases}$$

neglect 1 $\Rightarrow \frac{\omega_u}{\omega}$

or

$$|U(j\omega)| \approx \begin{cases} \frac{\omega_u}{\omega} \rightarrow \omega \gg \frac{\omega_u}{k} \rightarrow \text{High freq.} \\ k \rightarrow \omega \ll \frac{\omega_u}{k} \rightarrow \text{low freq.} \end{cases}$$

Summary

→ The dc gain of the transfer function is 'k'
[Expected]

→ It has a single pole at ' $\frac{\omega_u}{k}$ ' → pole freq.

→ Mag. plot :- $\omega \ll \frac{\omega_u}{k} \Rightarrow |U(j\omega)| = k$

Low freq. $\omega \gg \frac{\omega_u}{k} \Rightarrow |U(j\omega)| = \frac{\omega_u}{\omega}$ → Rolls off at 1st order [20 dB/dec]

→ Phase plot :- High freq.
Phase lag = $-\pi/4$ at pole freq. | phase lag = $-\pi/2$ at very high freq.