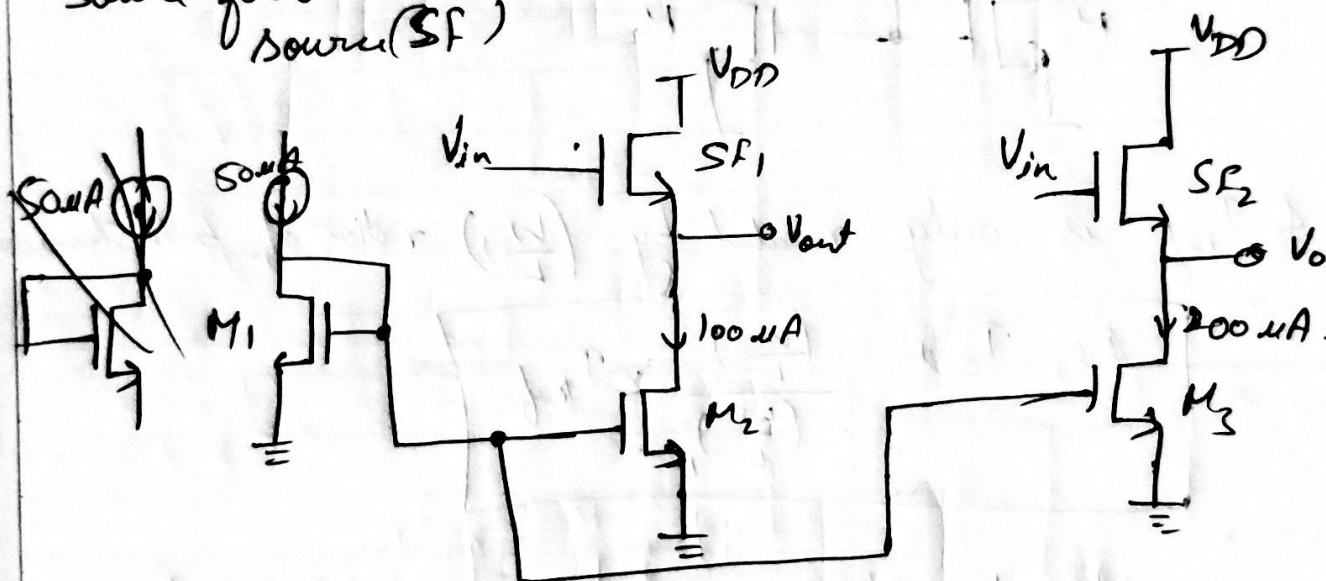


Examples:-

→ A circuit include two source followers biased at $100 \mu A$ & $200 \mu A$. We have a reference current of $50 \mu A$.

Ans Source follower:- Output at source & biased with a current source (SF)



$$I_{out} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} \times I_{ref}$$

$$100 \mu A = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} \times 50 \mu A$$

$$\left(\frac{W}{L}\right)_2 = 2 \times \left(\frac{W}{L}\right)_1$$

So,

$$\left(\frac{W}{L}\right)_2 = 2 \times \left(\frac{W}{L}\right)_1$$

$$\left(\frac{W}{L}\right)_3 = 4 \times \left(\frac{W}{L}\right)_1$$

$$200 \mu A = \frac{\left(\frac{W}{L}\right)_3}{\left(\frac{W}{L}\right)_1} \times 50 \mu A$$

$$\left(\frac{W}{L}\right)_3 = 4 \times \left(\frac{W}{L}\right)_1$$

* Alternative Perspective

EXPT. NO. NAME


M T W T F S S

Page No.

Date

YOUVA

In sat:-

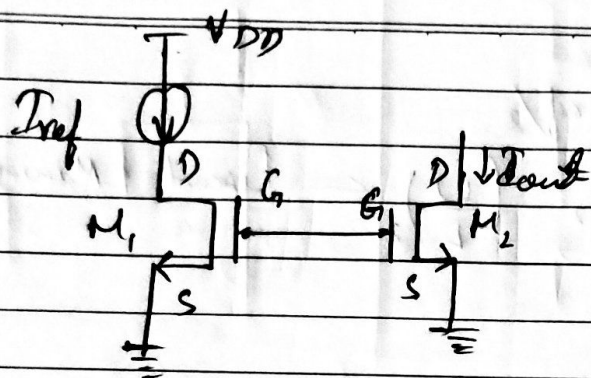


$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{th})^2$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 (V_{GS} - V_{th})^2$$

$$\left(\frac{I_{D2}}{I_{D1}} \right) = \left(\frac{W/L}{W/L} \right)_2$$

Example:-

Determine Iout

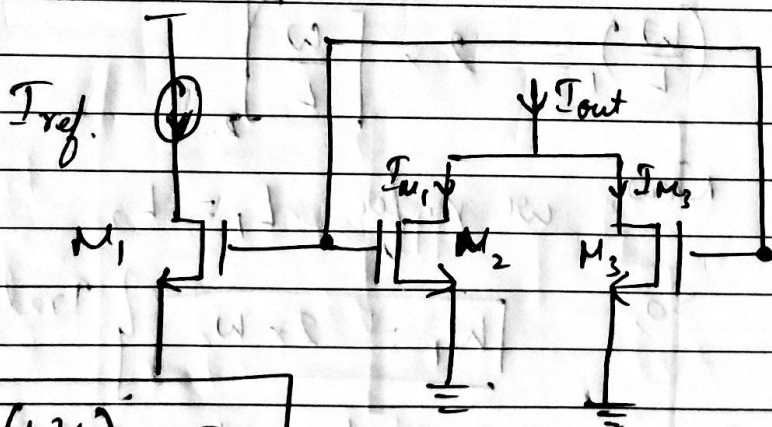

$$I_{M2} = \frac{(W/L)_2}{(W/L)_1} \times I_{ref}$$

$$I_{M3} = \frac{(W/L)_3}{(W/L)_1} I_{ref}$$

So,

$$I_{out} = I_{M2} + I_{M3}$$

Now, if M_1, M_2 & M_3 are identical


So,

$$I_{out} = 2I_{ref}$$

$$I_{out} = \frac{I_{ref}}{(W/L)_1} \left[(W/L)_2 + (W/L)_3 \right]$$

Teacher's Signature:

Quiz

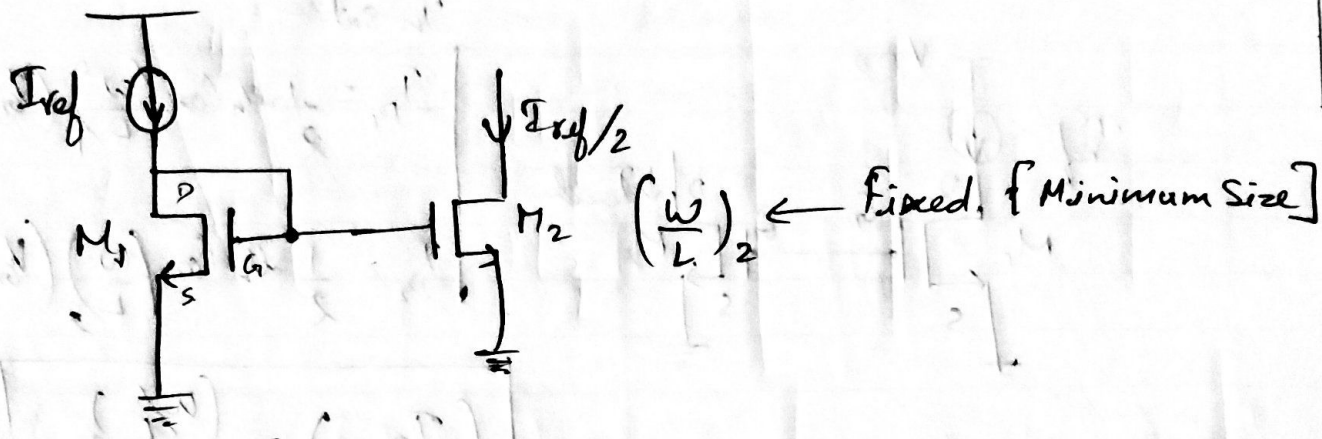

$$\frac{I_{ref}}{2} = \frac{(\frac{W}{L})_2}{(\frac{W}{L})_1} \times I_{ref}$$

$$(\frac{W}{L})_1 = 2 \times (\frac{W}{L})_2$$


Now, we prefer $L_1 = L_2$


So,

$$W_1 = 2 \times W_2 \quad \left. \vphantom{W_1 = 2 \times W_2} \right\} \text{Traditional method.}$$

Since we have to make $(\frac{W}{L})_2$ fixed


So,

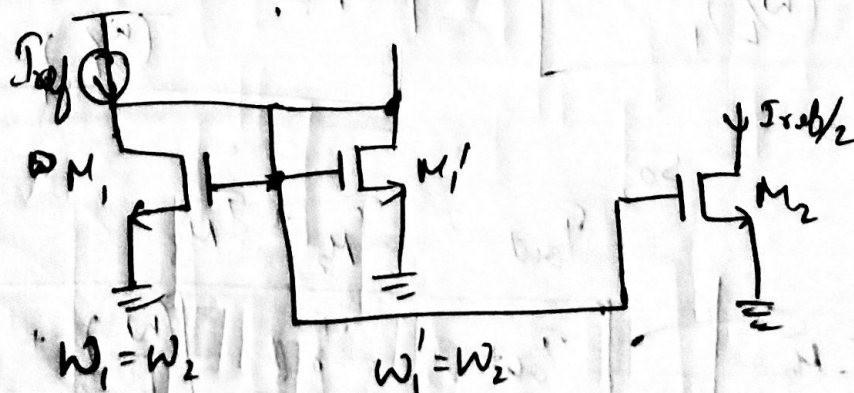

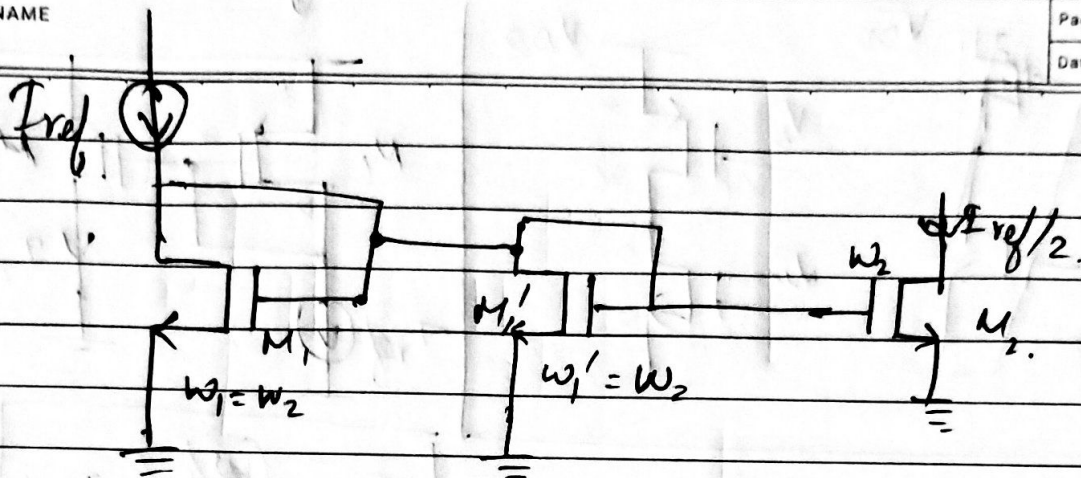

→ When we put 2 transistors in parallel, they behave like their width becomes double (if they have same width), as you can see in the above example.




* Proper Scaling

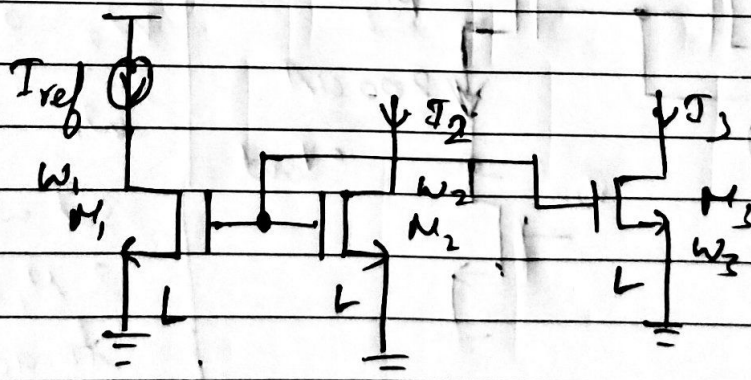

→ Always choose the same L , only scale w :

$$\left(\frac{w_2}{w_1}\right) I_{ref} = I_2 \quad \left| \quad \left(\frac{w_3}{w_1}\right) I_{ref} = I_3.$$


* PMOS Current Mirror

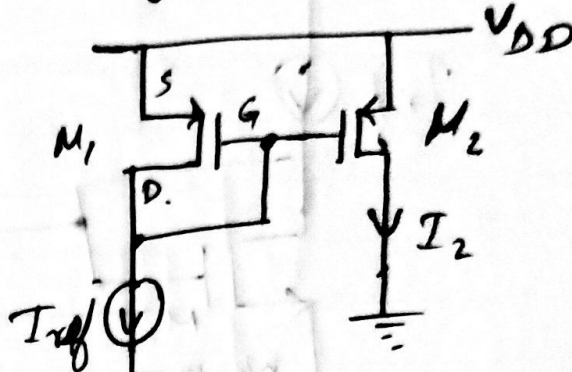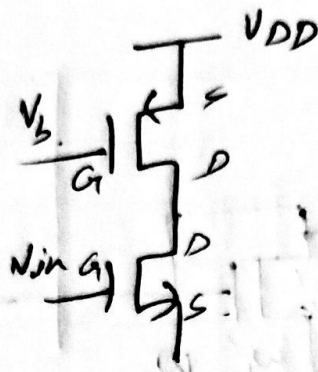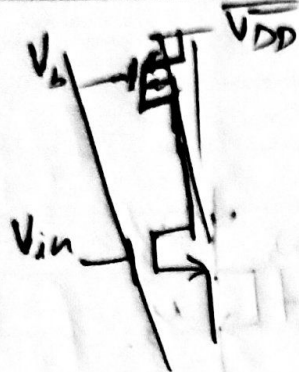

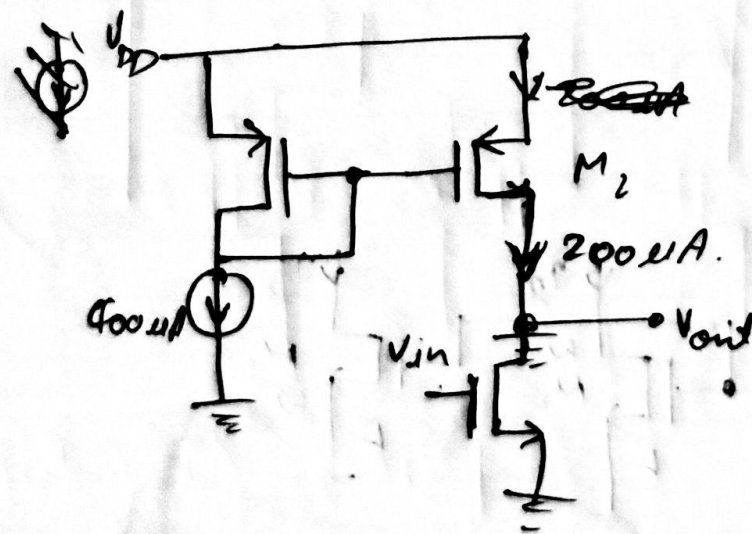Example

An NMOS common source stage requires a load current source equal to $200\mu A$. We have a reference current equal to $400\mu A$.

$$I_2 = \frac{(W/L)_2}{(W/L)_1} I_{ref}$$



Traditional method

$$L_1 = L_2$$


$$W_2 = 0.5 W_1$$

$$W_1 = 2 W_2$$

But we'll use 2 M_1 s in parallel to achieve the result


Actual circuit

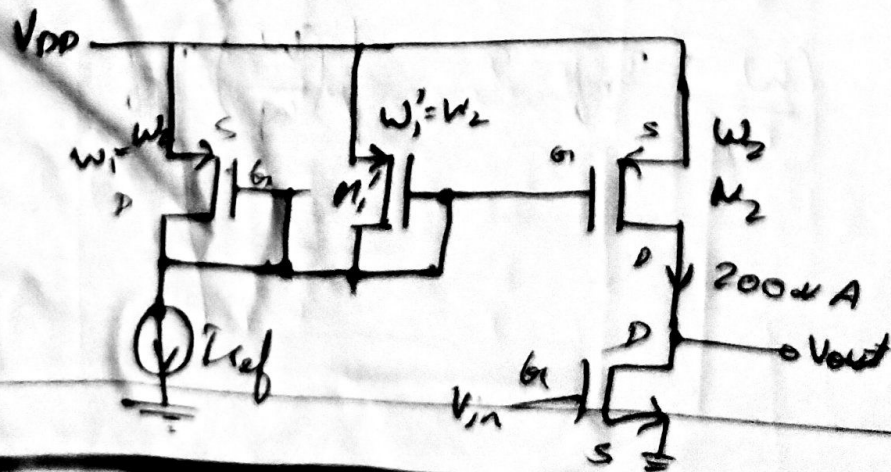→ 2 unit devices [PMOS]
→ so same W & L .



* Bipolar Current Mirrors

EXPT. NO.	NAME	M T W T F S S	Page No.:	YOUVA
			Date	

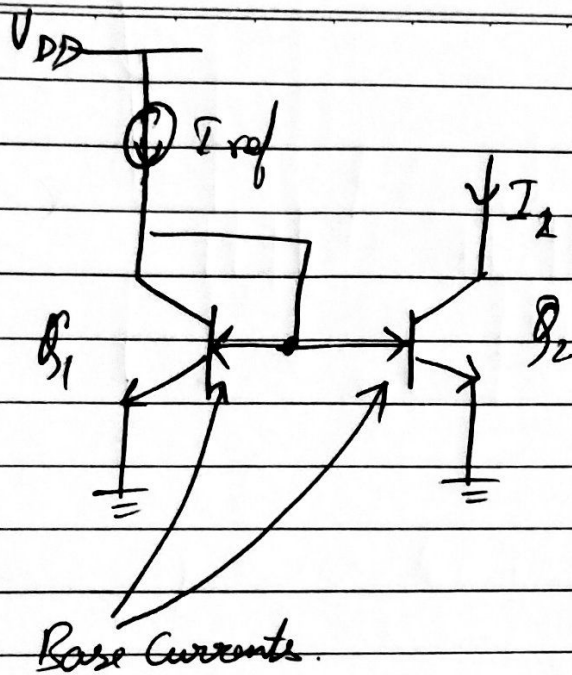


$$I_{C1} = I_{S1} \exp\left\{\frac{V_{BE}}{V_T}\right\}$$

$$I_{C2} = I_{S2} \exp\left\{\frac{V_{BE}}{V_T}\right\}$$

$$\frac{I_{C2}}{I_{C1}} = \frac{I_{S2}}{I_{S1}}$$

→ If I_{S1} & I_{S2} are identical

Problem:-

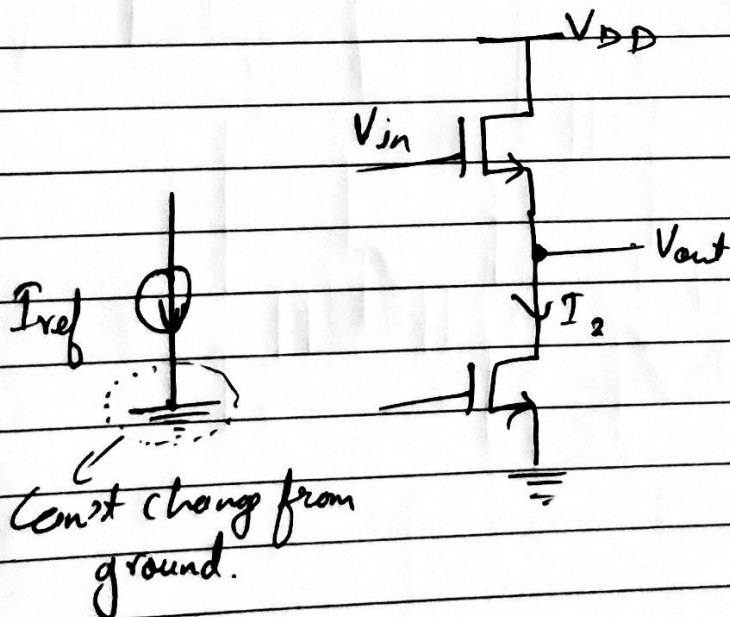

How to use I_{ref} so I_2 is a good copy of I_{ref} ?