
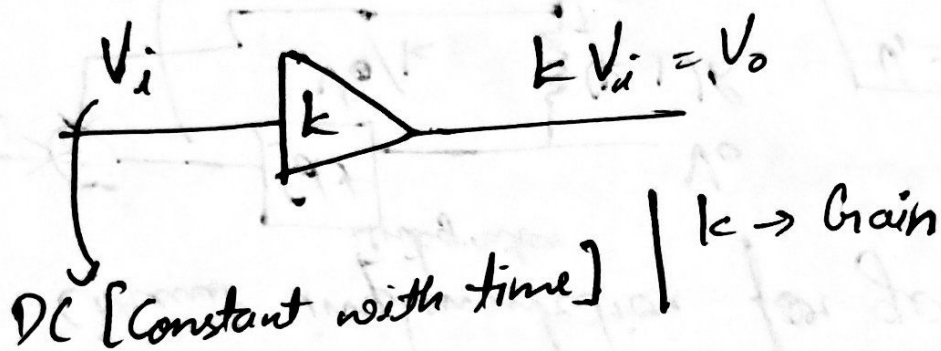



* Negative Feedback amplifier

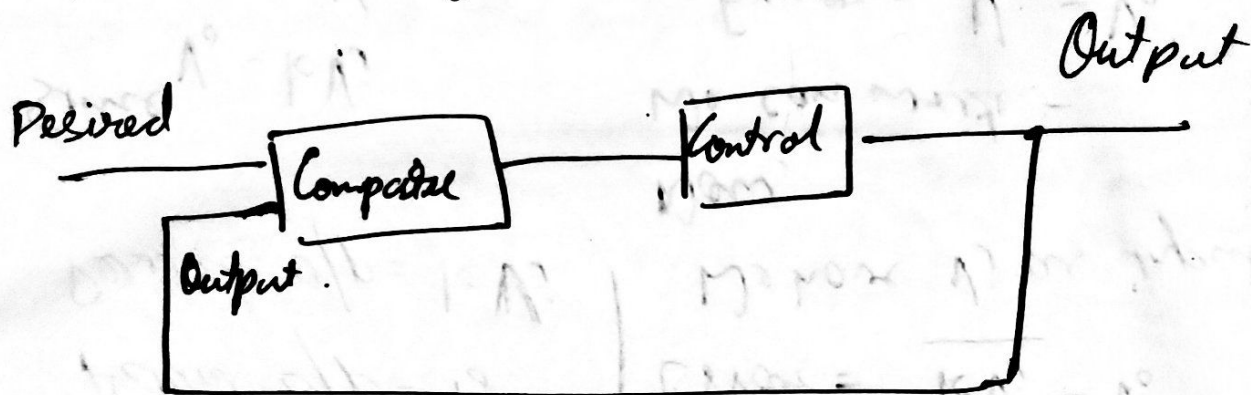

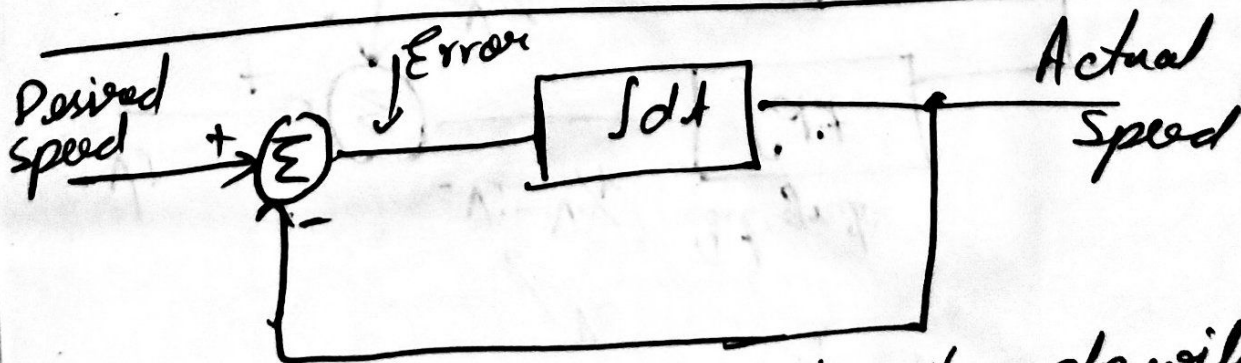Example [Feedback system]




Negative Feedback :- Compare the desired & actual outputs to compute the error.
 \rightarrow Control the output in a direction that reduces the error.



When error = 0 \rightarrow Integrator o/p will be constant.

Amplifier using negative feedback

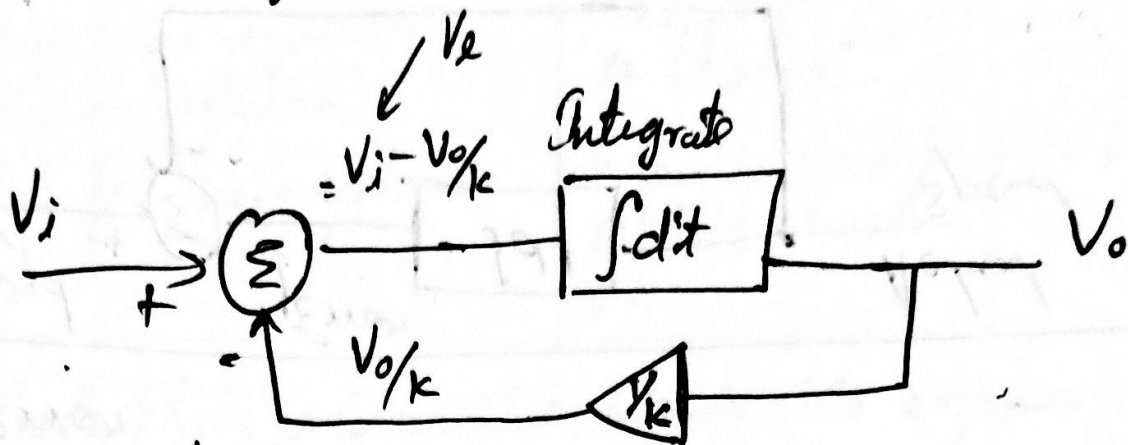

$$V_o = k V_i$$

↘ Gain

$V_i \rightarrow d.c.$

Compare actual o/p to the desired o/p

Actual o/p = V_o

Desired o/p = $k V_i$

$$\text{Error} = k V_i - V_o$$

We have V_i as input.

Now,


We can write :-

$$\text{Error} = V_i - \frac{V_o}{k}$$

Since $V_o = k V_i$

$$V_i = \frac{V_o}{k}$$

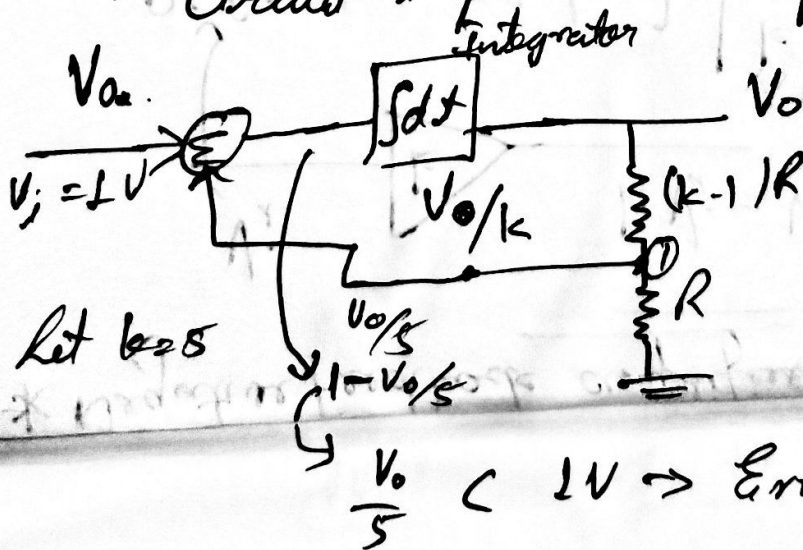Now, circuit implementation for getting $\frac{V_o}{k}$ from



$$V_i = \frac{V_o \times R}{(k-1)R + R}$$

$$= \frac{V_o \times R}{kR} = \frac{V_o}{k}$$

$$\frac{V_o}{5} < 1V \rightarrow \text{Error} > 0.$$

$$\frac{V_o}{s} = 1V \rightarrow \text{Error} = 0$$


Now, output V_o is constant if error $= 0$

Negative feedback Amplifier:-

↳ Basic principle:- Integrate the error to drive the output.

$$\frac{V_o}{1s} = V_i$$


$$V_o = k V_i$$

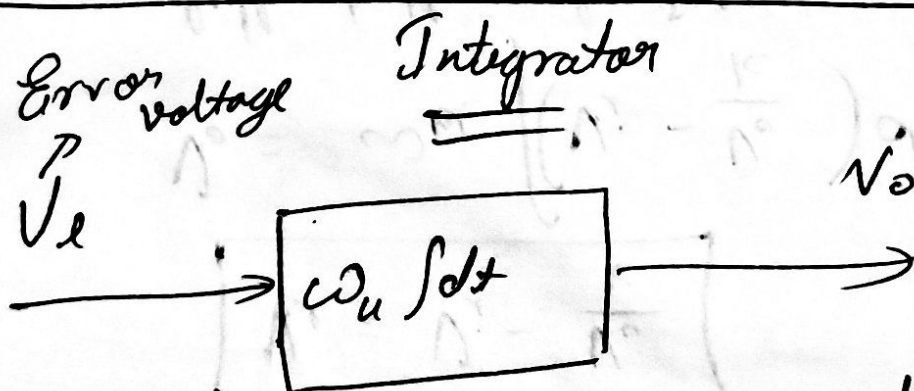

$\omega_u \rightarrow$ Constant for dimension frequency

$$V_o = \omega_u \int V_e \cdot dt$$

$$V_e = 1V$$

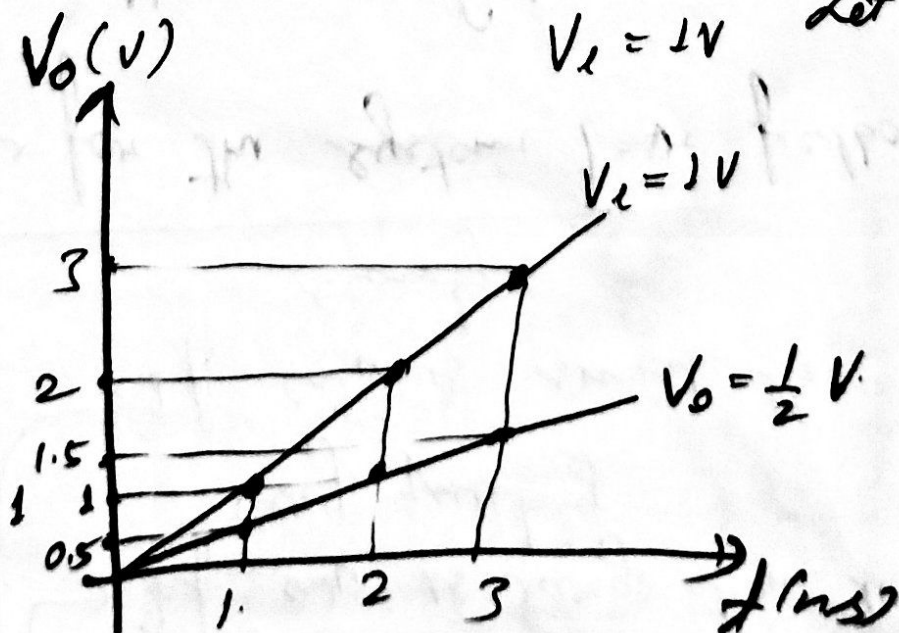

$\omega_u \rightarrow$ Freq dimension of freq.

Let $\omega_u = 1 \text{ Grad/s}$

$$= 10^9 \text{ rad/s}$$

$$V_o = 10^9 \int 1 dt$$

$$= 10^9 t$$

$\omega_u \rightarrow$ proportionality constant

→ The speed of integration defines by ω_u .

Proportionality condition:-

→ If ω_u is large then integrator integrates very quickly

→ If ω_u is small then integrator integrates slowly.

Now for the system [-ve feedback amp.]

$$V_o = \omega_u \int V_e dt$$

$$\boxed{V_e = V_i - \frac{V_o}{k}}$$

$$V_o = \omega_u \int \left(V_i - \frac{V_o}{k} \right) dt$$

diff. both sides [this will be easy]

$$\frac{dV_o}{dt} = \omega_u \left[V_i - \frac{V_o}{k} \right]$$

1st order diff. eqⁿ

$$\frac{dV_o}{\left(V_i - \frac{V_o}{k} \right)} = \omega_u dt \quad \left. \vphantom{\frac{dV_o}{\left(V_i - \frac{V_o}{k} \right)}} \right\} \begin{array}{l} \text{Integrate} \\ \text{Rearrange} \end{array}$$

$$\frac{dV_o}{kV_i - V_o} = \frac{\omega_u dt}{k}$$

Integrating

$$-\ln(kV_i - V_o) \Big|_{V_o(0)}^{V_o(t)} = \frac{\omega_u}{k} t \Big|_0^t$$

$$\ln \left[\frac{kV_i - V_o(0)}{kV_i - V_o(t)} \right] = \frac{\omega_u}{k} \cdot t$$

$$\ln \left[\frac{kV_i - \overset{\text{or}}{V_o(t)}}{kV_i - V_o(0)} \right] = -\frac{\omega_u}{k} \cdot t$$

Now,

$$\boxed{V_o(t) = V_o(0) \exp\left[-\frac{\omega_u}{k} \cdot t\right]}$$

→ Solution to the 1st order differential equation.

$$\boxed{V_o(t) = V_o(0) \cdot \exp\left(-\frac{\omega_u}{k} \cdot t\right) + kV_i \left[1 - \exp\left(-\frac{\omega_u}{k} \cdot t\right)\right]}$$

$$\cancel{V_o(t)} = kV_o = kV_i \rightarrow \text{when } t = \infty$$

Let say initial condition of output is 0, i.e. $V_o(0) = 0$

$$\text{So, } V_o(t) = \underline{k V_i \left[1 - \exp\left(-\frac{\omega_u t}{k}\right) \right]}$$

$$= 0.99 \cdot \underbrace{k V_i}_{\text{Ideal value}} \rightarrow 99\% \text{ of the ideal value}$$

So,

$$1 - \exp\left(-\frac{\omega_u t}{k}\right) = 0.99$$

$\frac{k}{\omega_u}$ } time
Constant

$$\exp\left(-\frac{\omega_u t}{k}\right) = 0.01 \rightarrow 1\%$$

$$\text{So, } \boxed{t = 2 \ln(10) \cdot \frac{k}{\omega_u}} \rightarrow \text{dim(freq)}$$

$$\text{So, } \frac{k}{\omega_u} \text{ } \} \text{dim(time)}$$

~~So, $t = 2 \ln(10) \cdot \frac{k}{\omega_u}$ for $k = 5$
 $V_i = 1V$~~

⑧

$$\omega_u = 10^6 \text{ rad/s}$$

$$k = 5$$

$$\text{So, } \exp\left(-\frac{\omega_u t}{k}\right) = 0.01$$

$$t = 2 \ln(10) \cdot \frac{k}{\omega_u}$$

$$t = \frac{k}{\omega_u} = \frac{5}{10^6} = 5 \times 10^{-9} \text{ s} = 5 \text{ ns}$$

$$\text{So, } t = 2 \times \ln(10) \times 5 \text{ ns}$$

$$= 23 \text{ ns}$$

$$= \underline{\underline{23 \text{ ns.}}}$$

this time o/p will take
to reach 99% of the steady state value
[k V_i] } for zero initial condition.

⑧

$\omega_u = 5 \text{ Grad/s} \rightarrow$ faster integrator.

$$k = 5$$

$$\text{So, } \exp\left(-\frac{\omega_u}{k} t\right) = 0.01$$

$$\frac{k}{\omega_u} = \frac{5}{5 \times 10^9} = 1 \text{ ns}$$

$$\text{So, } t = 2 \ln(10) \cdot \frac{k}{\omega_u} = 2 \times \ln(10) \cdot 1 \text{ ns} \\ = \underline{\underline{4.6 \text{ ns.}}}$$

\rightarrow For high speed amp. you need high speed
integrator also