
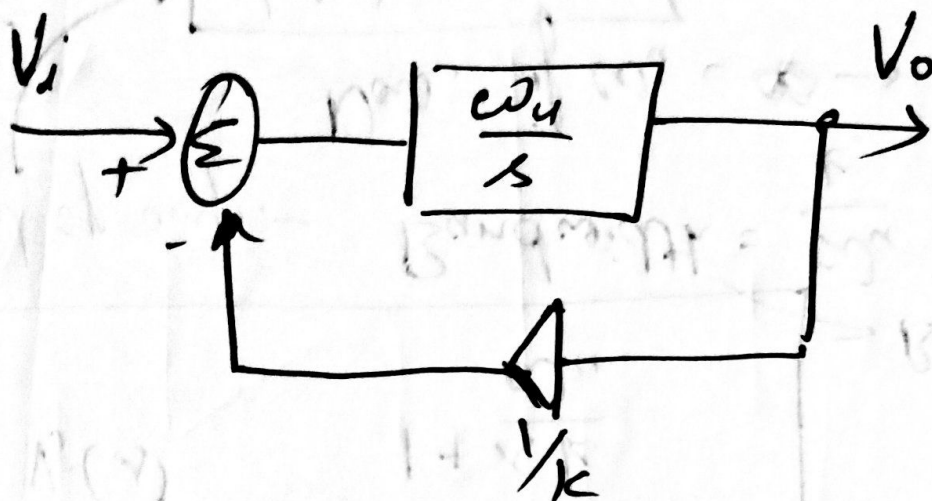


Negative feedback Amp.:-

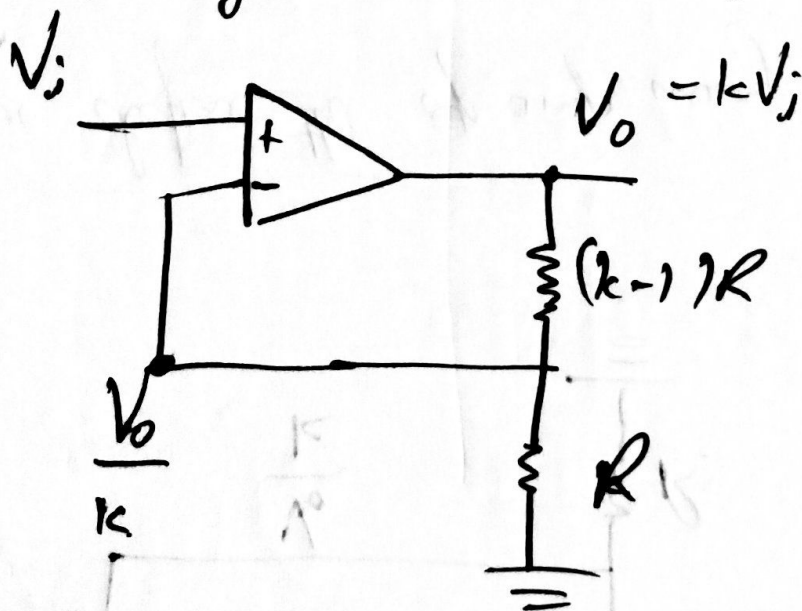


* Other amplifiers using an op-amp.

① VC VS [Voltage Controlled Voltage Source]



② CCVS [Current Controlled Voltage Source]



$$V_o = R_f \cdot I_i$$

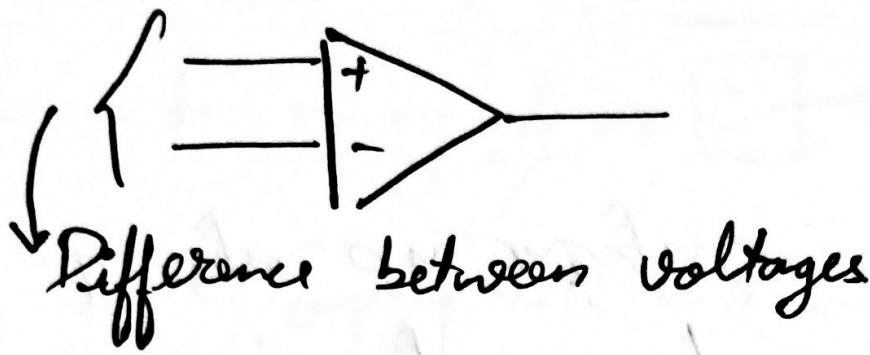


$$V_o = R_f I_i$$

$$V_o - R_f I_i > 0 \downarrow \text{Reduce } V_o$$
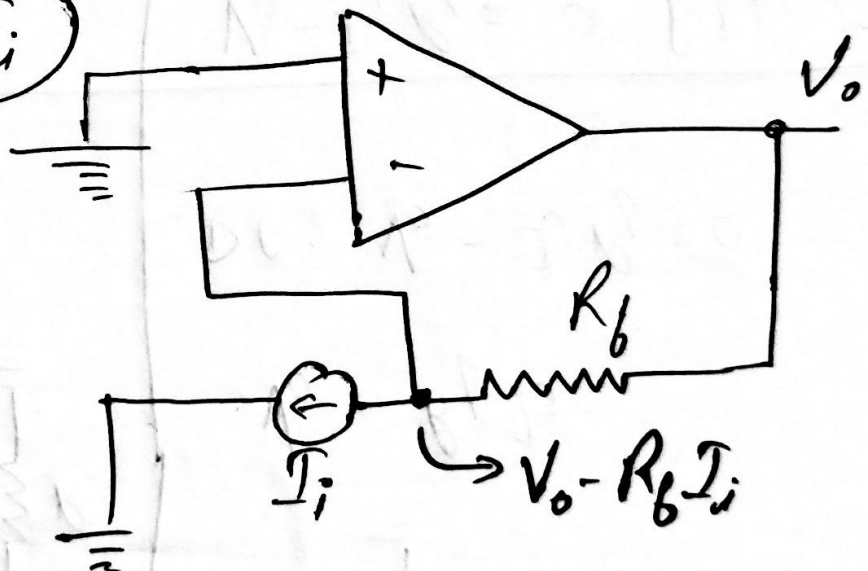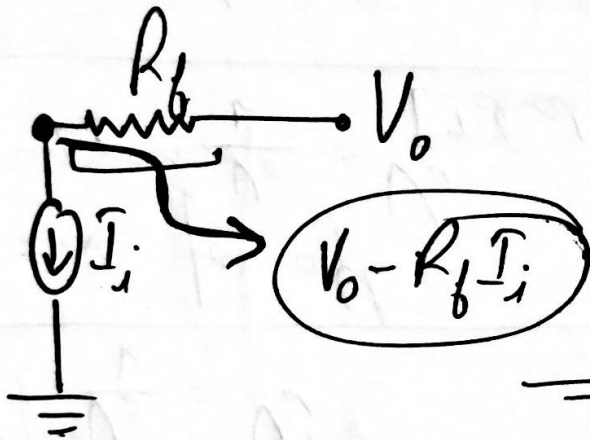
$$V_o - R_f I_i < 0 \downarrow \text{Increase } V_o$$




Familiar Way

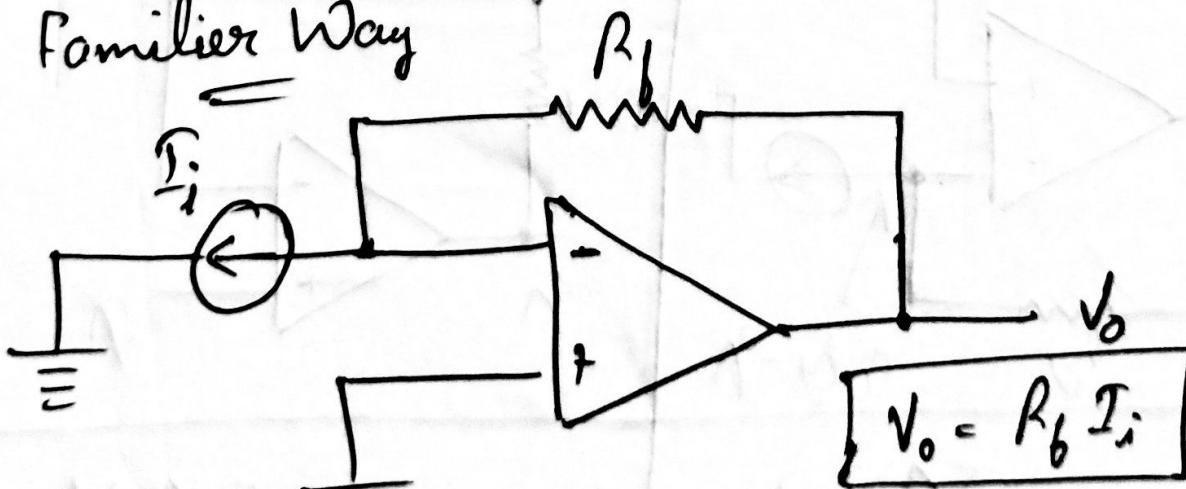

I_i (dc) \rightarrow The only way the output will reach a steady value by $V_o = R_f I_i$.

* Summary


V C V S

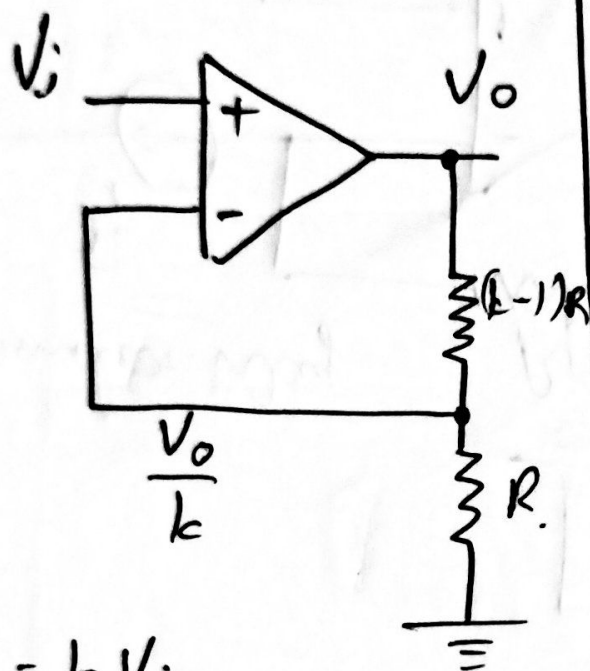

$$V_o = k V_i$$

DC: $\frac{V_o}{k} = V_i$

C C V S

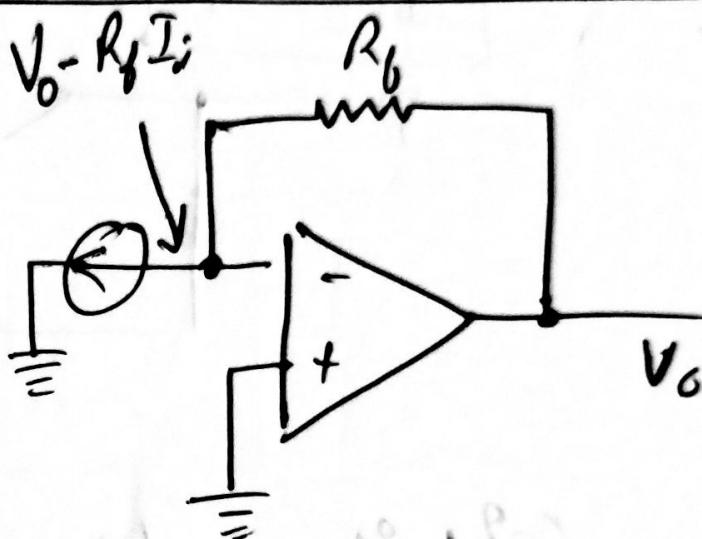

$$V_o = R_f I_i$$

DC: $V_o - I_i R_f = 0$

$\omega_n = \infty$ for all
freq. $\rightarrow \frac{V_o}{k} = V_i$ [Ideal]

$V_o - I_i R_f = 0$ [Ideal]



* How to design an op. amp?

① Design an integrator.


Integrator Realization

→ Integrator using $\frac{L}{\text{or}} \boxed{C}$ → Best choice

Impractical (Cause bulky)

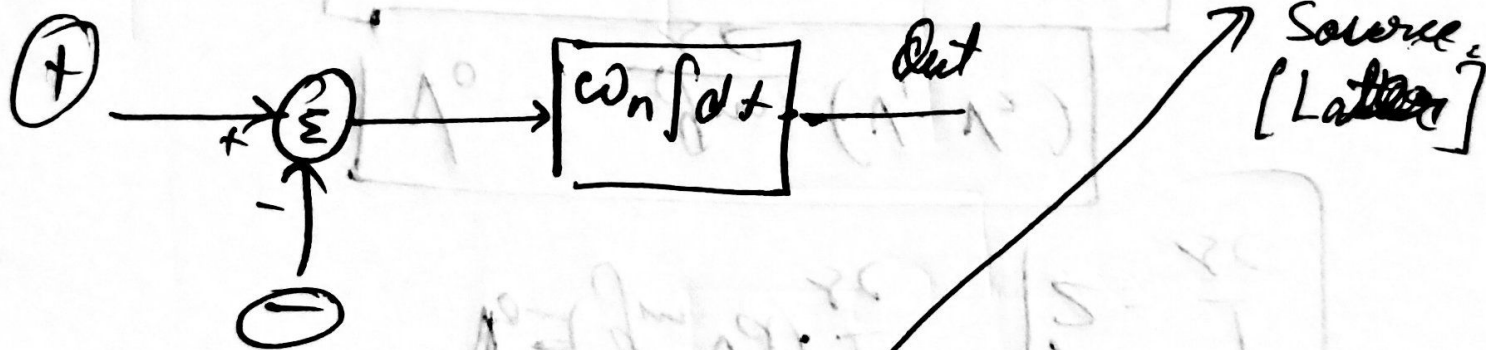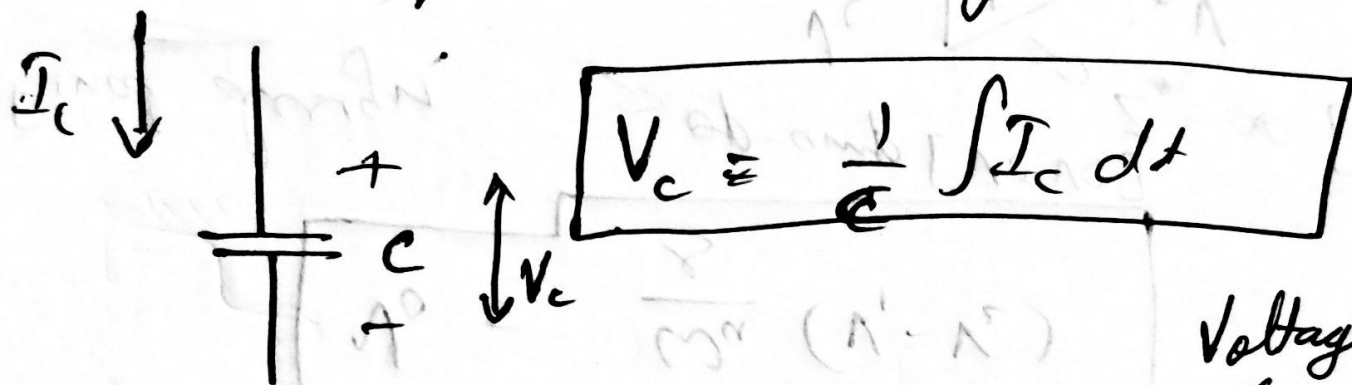

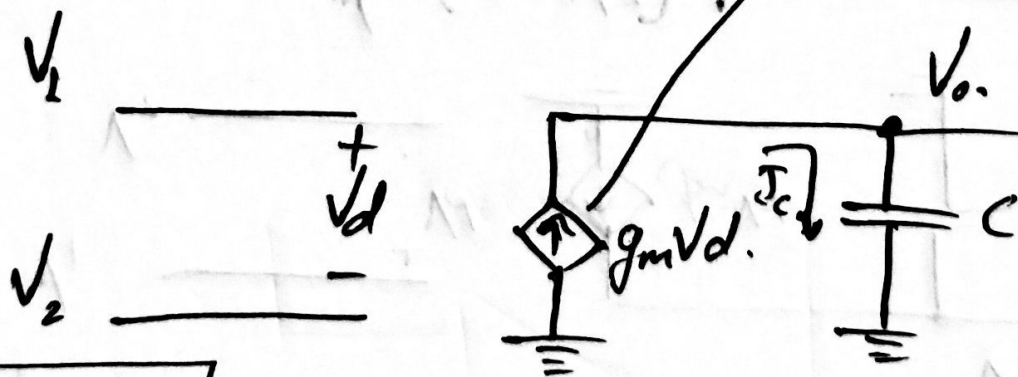Voltage Controlled
Current
Source
[Later]



$$V_d = V_1 - V_2$$

$$I_c = g_m V_d \quad \text{Now, } V_o = \frac{1}{C} \int I_c dt$$

$$\text{So, } \boxed{V_o = \frac{g_m}{C} \int (V_1 - V_2) dt} \quad \text{or } V_o = \frac{g_m}{C} \int V_d dt$$


So,

$$V_o = \omega_n \int (V_1 - V_2) dt$$

$$\omega_n = \frac{g_m}{C}$$

In frequency domain:-

$$V = IZ$$

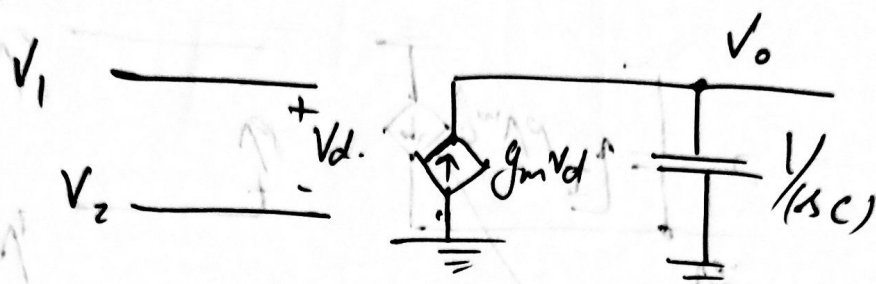

$$V_o = (g_m V_d) \frac{1}{sC}$$

$$Z = \frac{1}{sC}$$


$$V_o = \frac{g_m}{sC} (V_1 - V_2)$$

$$V_o = \frac{\omega_n}{s} (V_1 - V_2)$$

Final design

op-amp. [V_C V_S]

Z_{in} = ∞ [Buffer]

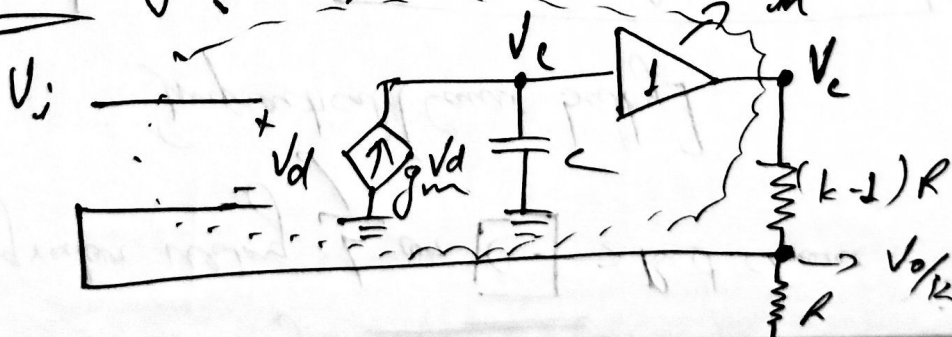

→ The voltage buffer is used to maintain the application of the design, if we don't use the buffer the some current will be drawn by the voltage divider used to get $(\frac{V_o}{k})$.